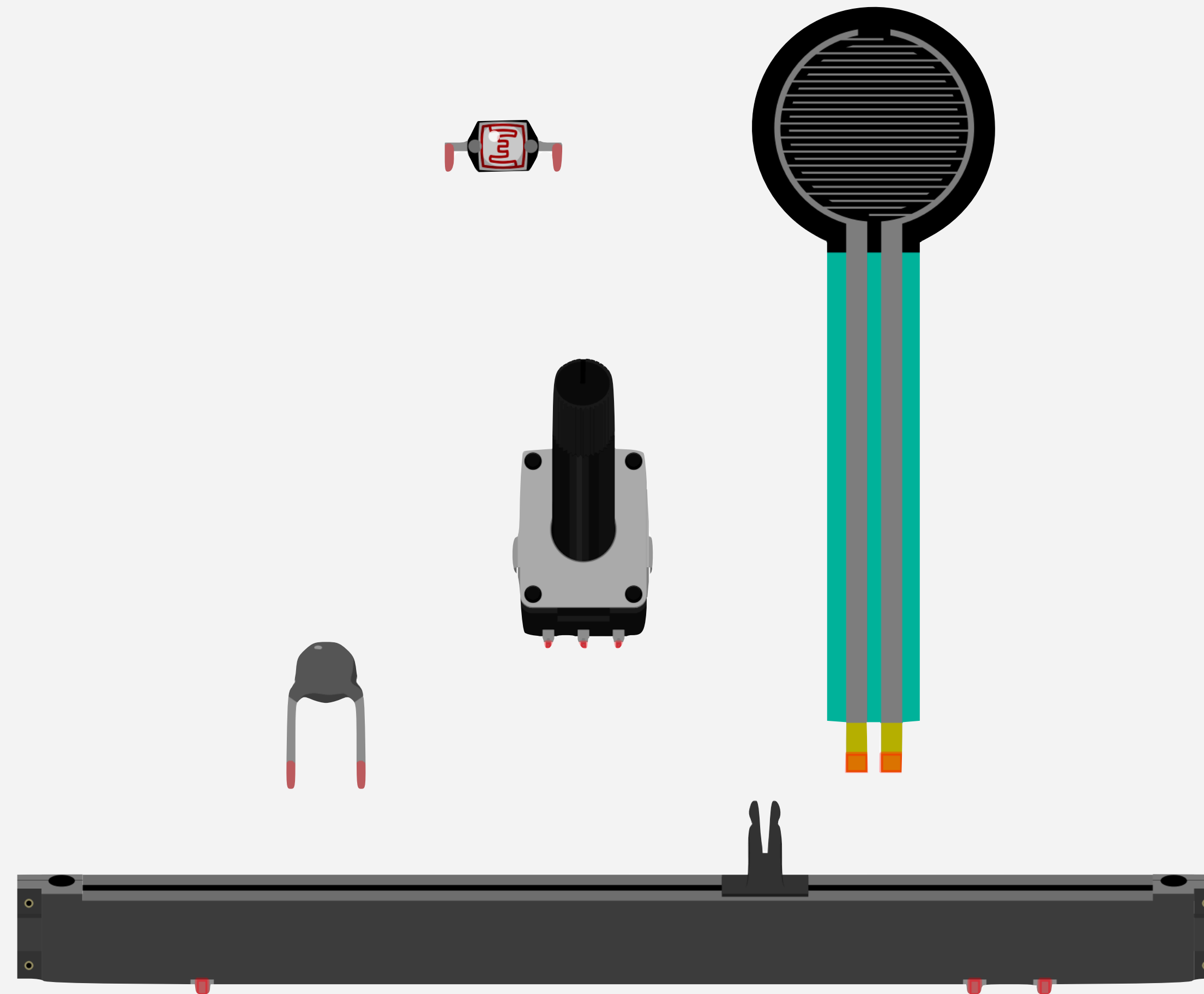


ANALOG INPUT





**Knobs, Sliders, Temperature,
Light, & more!**

Analog Input

An analog input is any device that can create or transmit a range of values beyond just on/off.

Using Analog Inputs with the Arduino

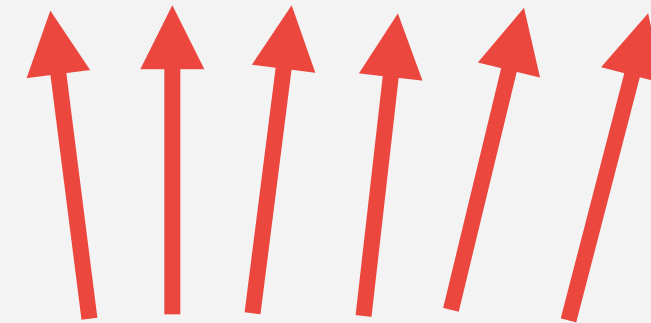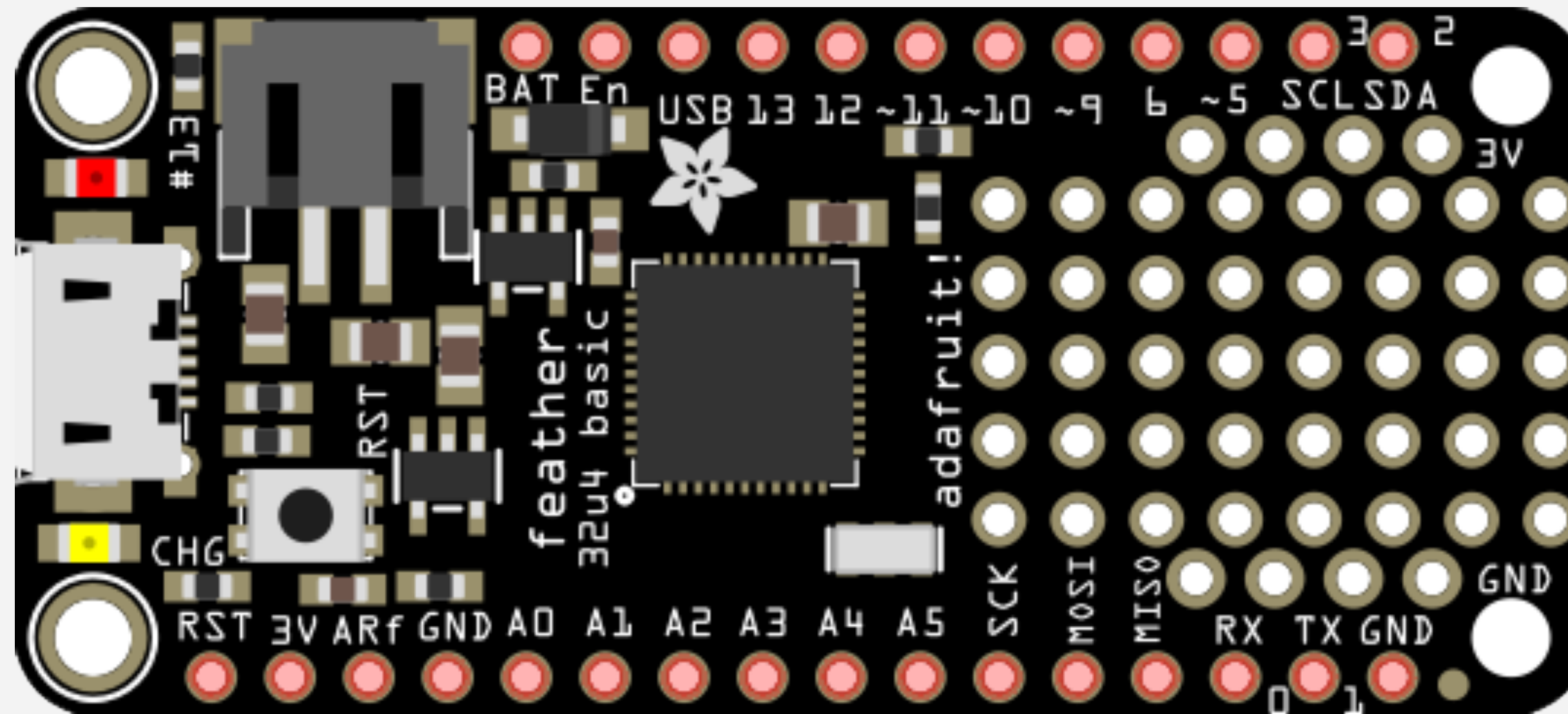

Analog Input Pins

Analog Input


The inputs on the Arduino read voltage.


All inputs need to be thought of in terms of voltage differentials.


Unlike digital inputs, analog inputs convert differences in voltage levels into a number from 0-1024


Analog Input

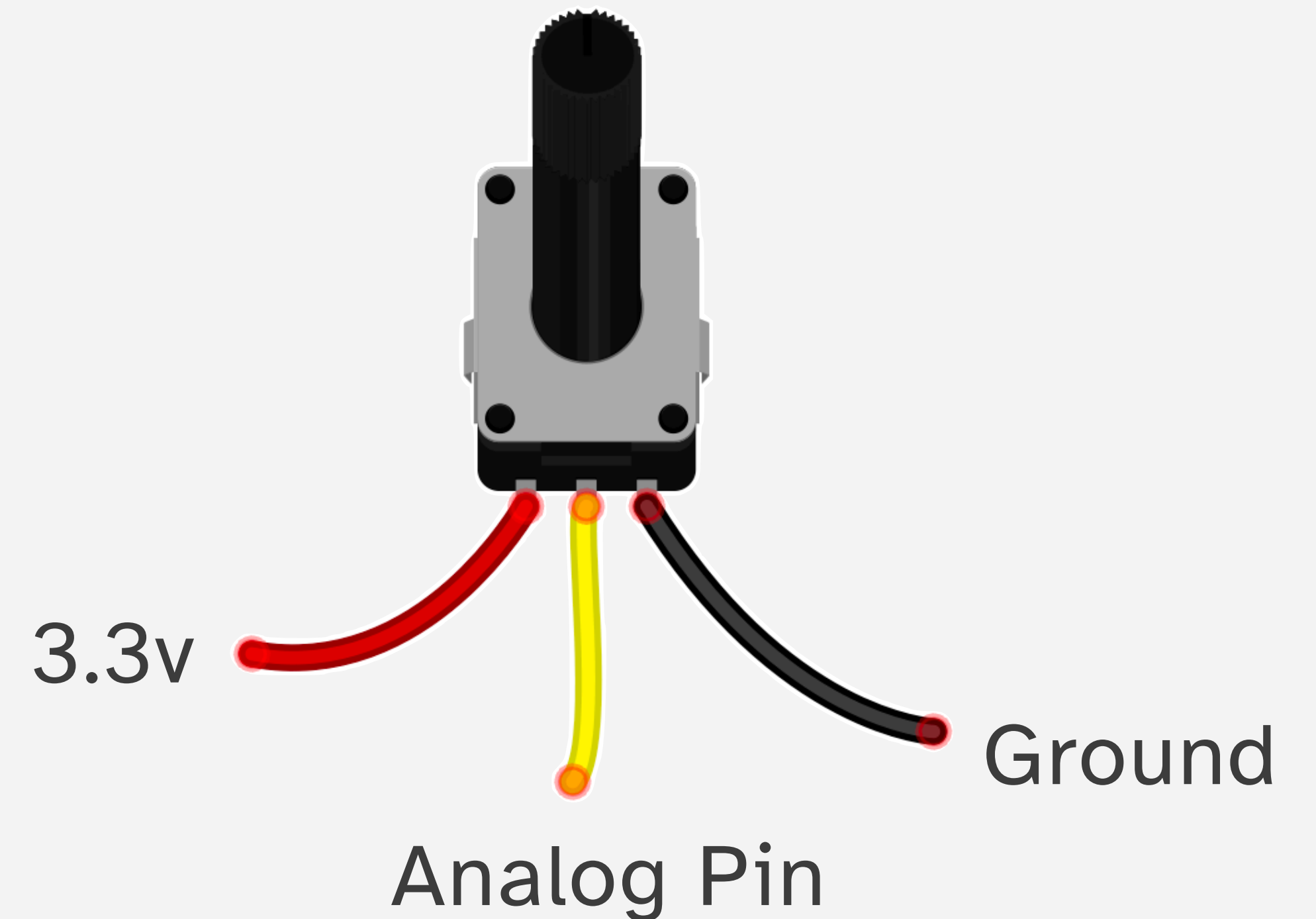
The potentiometer is the easiest analog input to use. It has three connections.



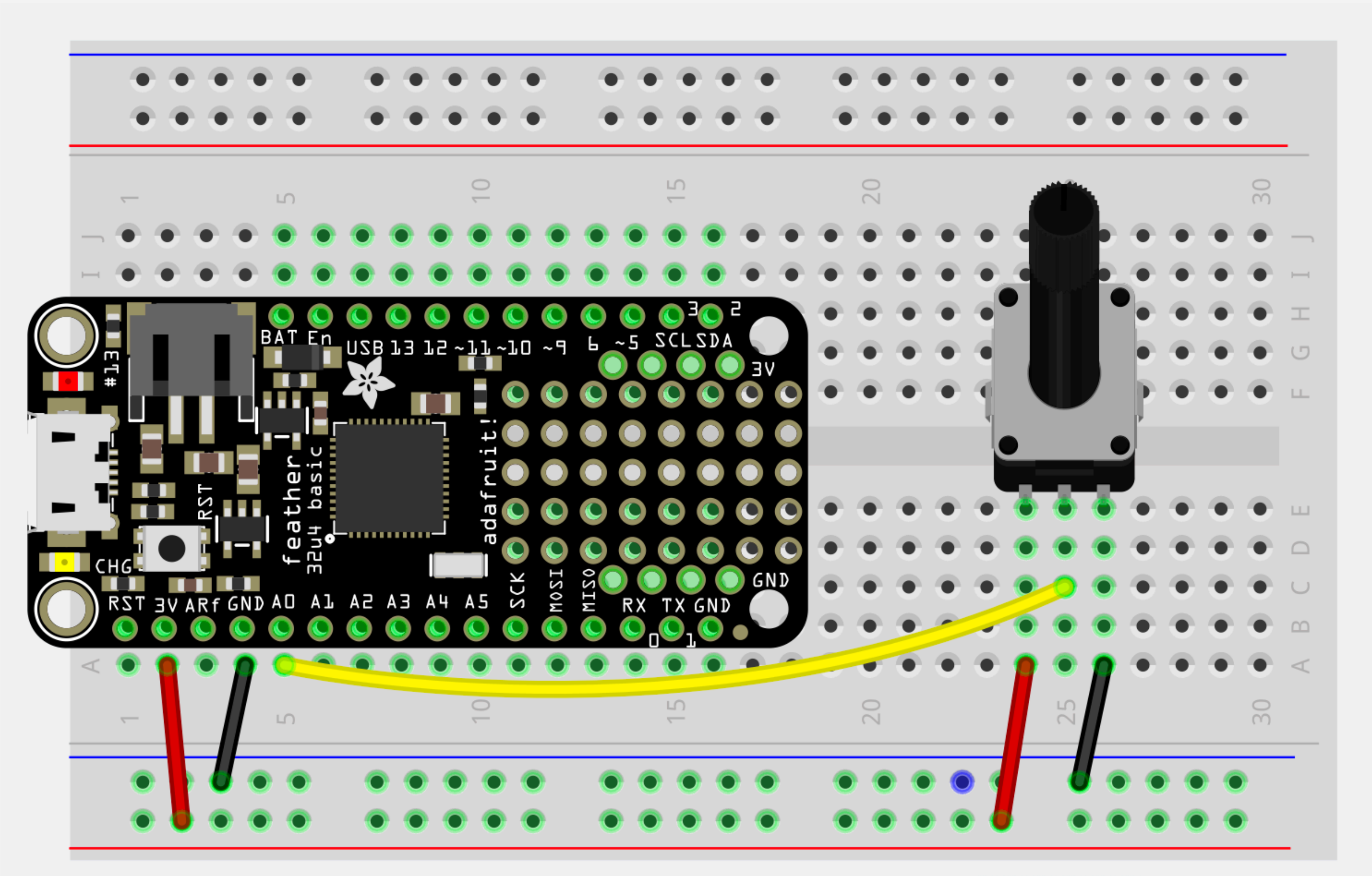

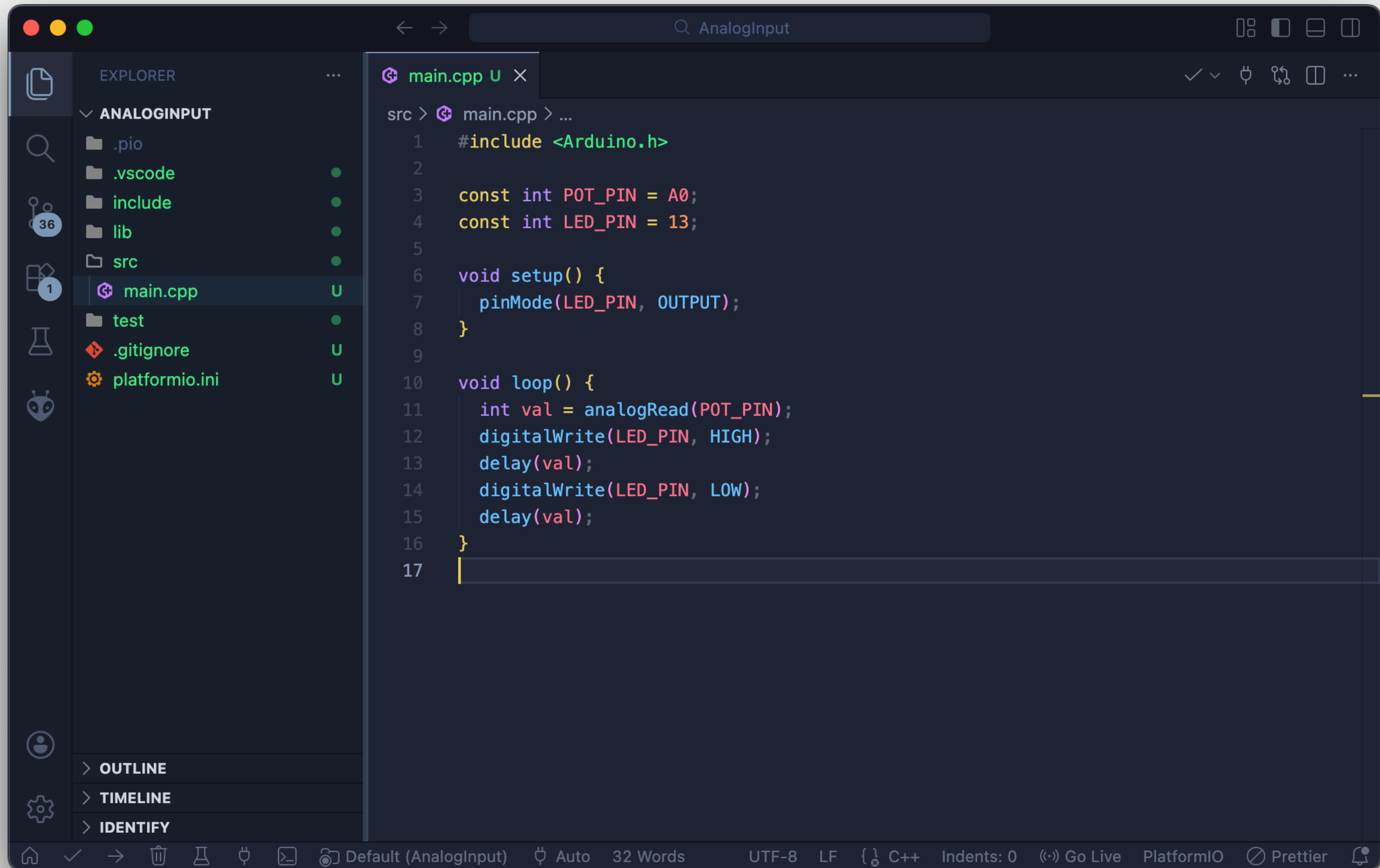


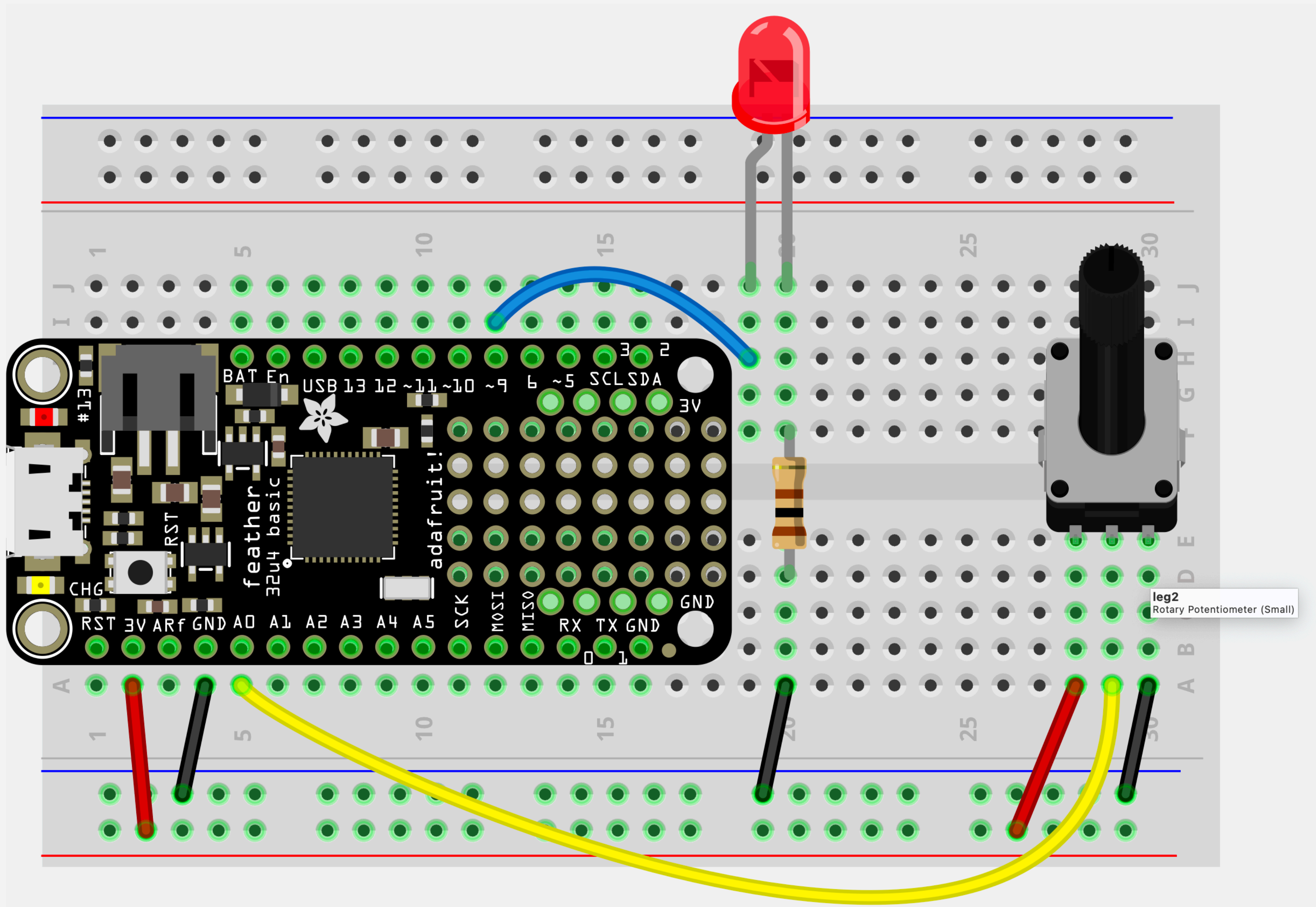

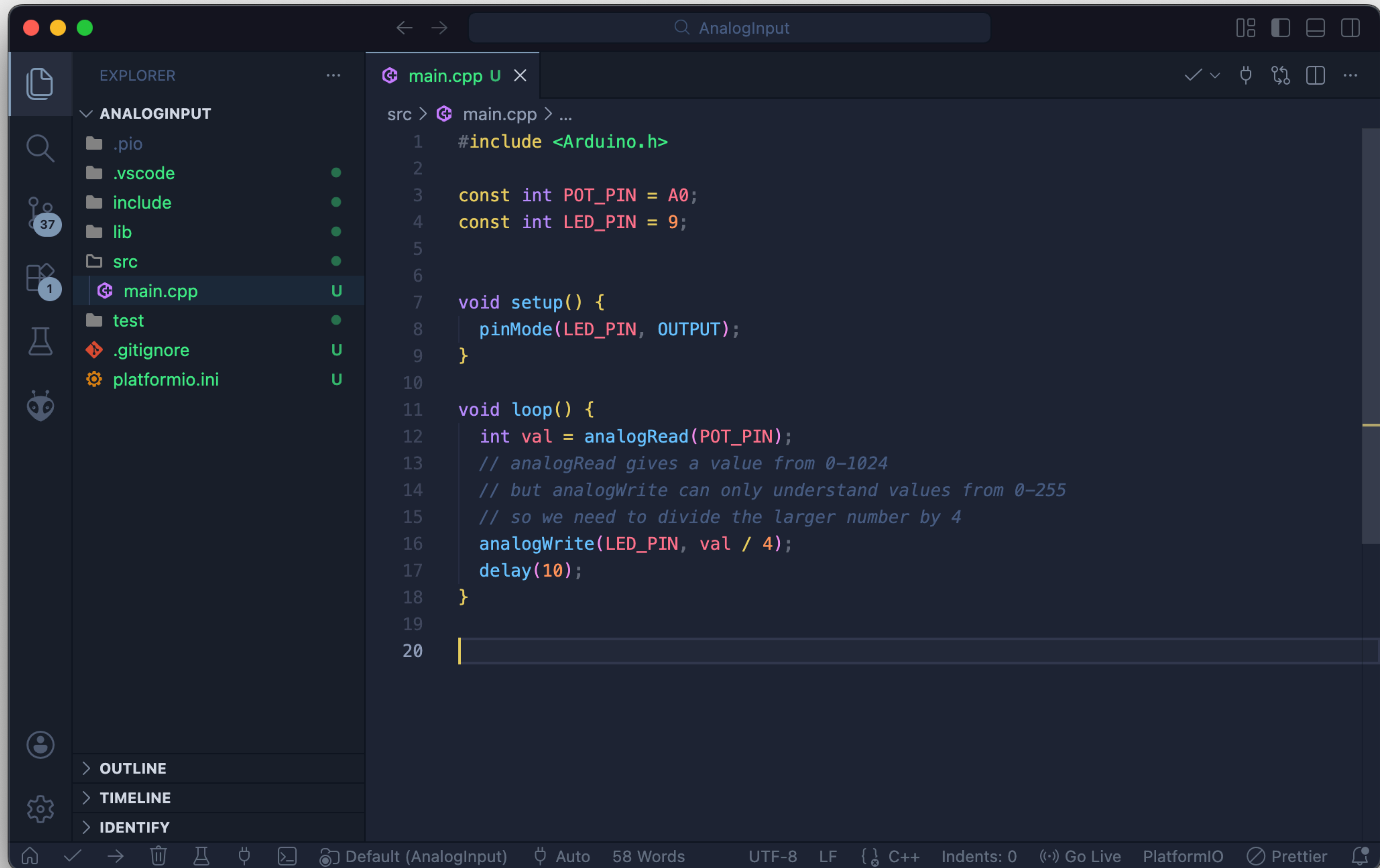


VOLTAGE DIVIDERS

Voltage Divider

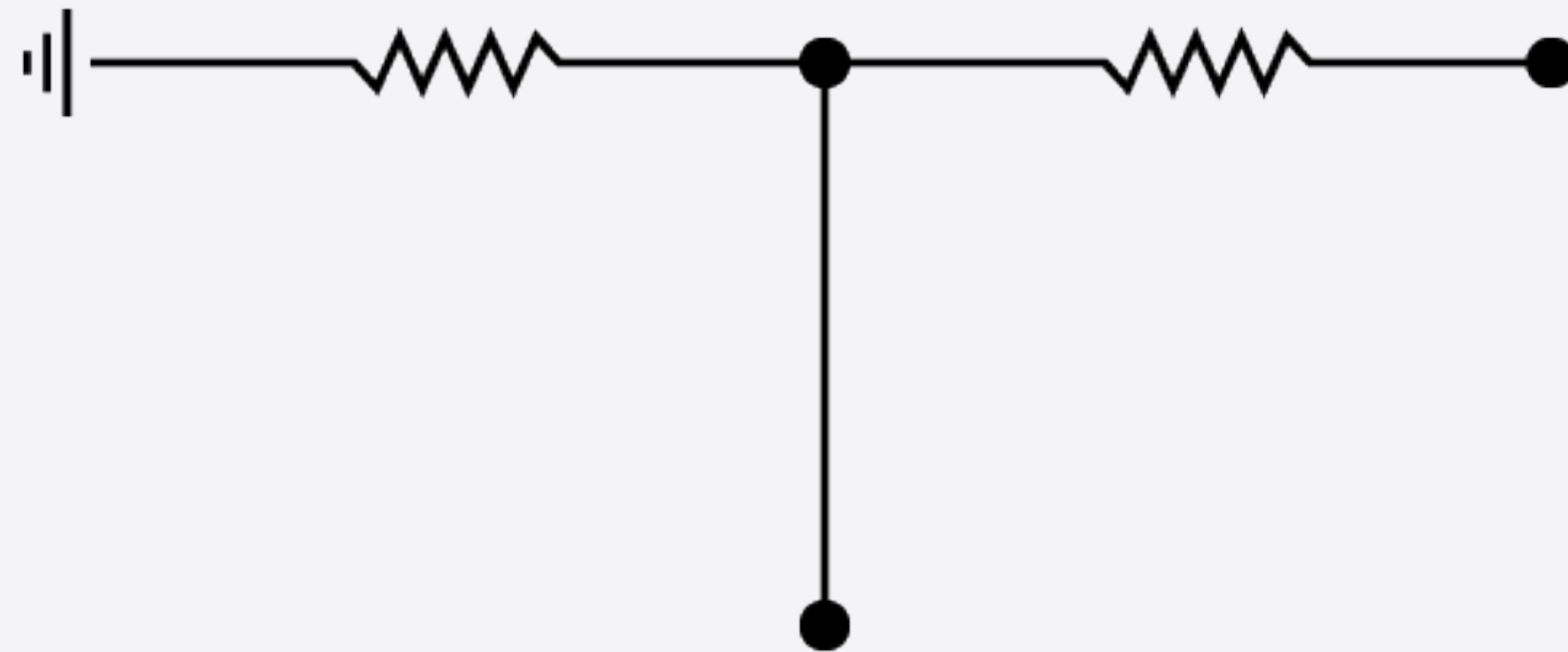


The Voltage Divider is a simple circuit that lets you convert a change in resistance into a change in voltage.

Voltage Divider

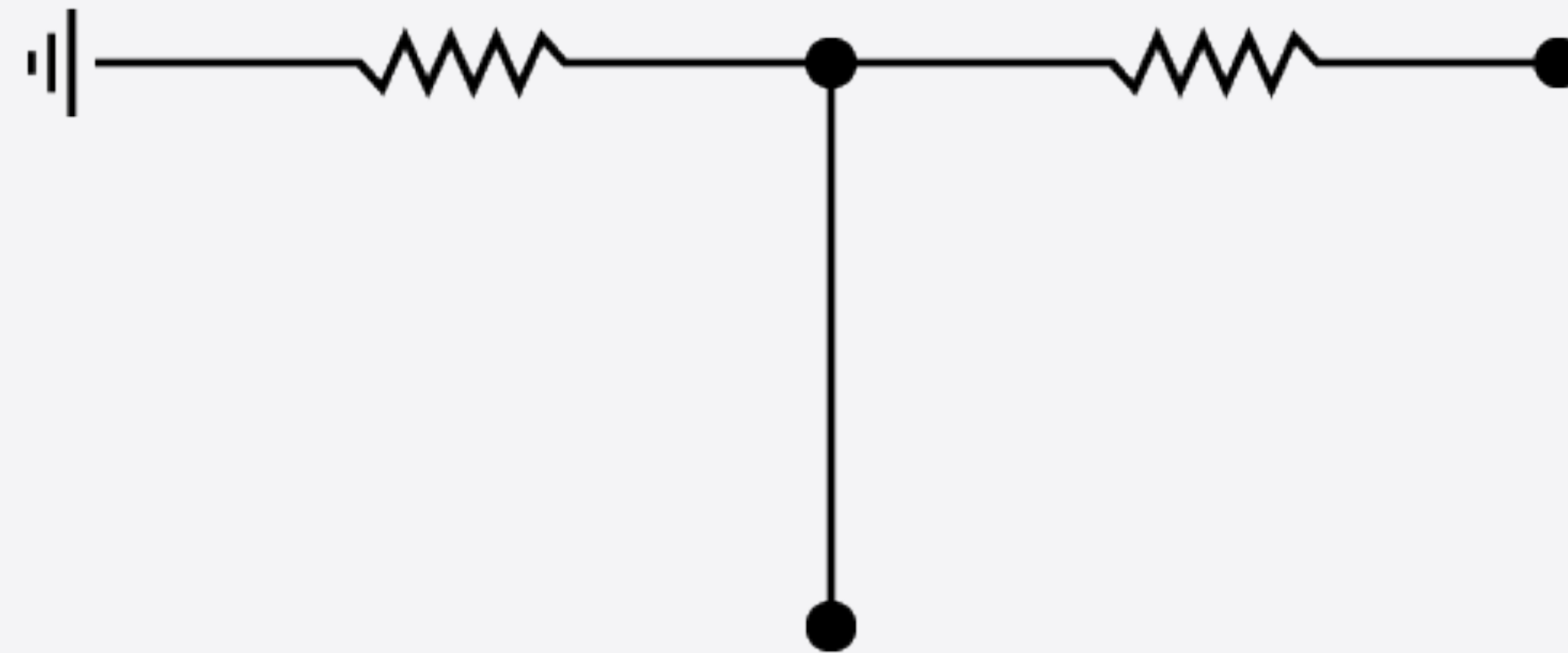

This is useful because there are a number of sensors that change resistance, but the Arduino can only sense changes in voltage.


Voltage Divider

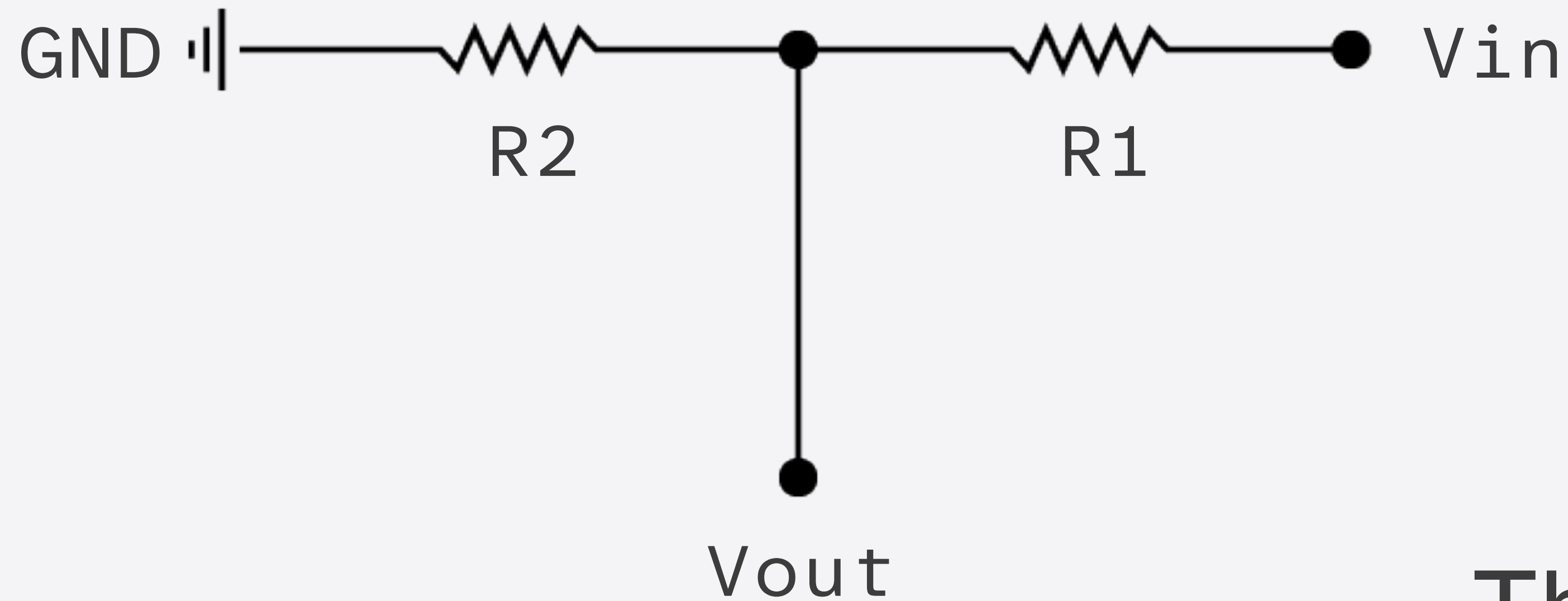

The resistor closest to ground is called R2.

The resistor closest to the input voltage (V_{in}) is called R1.

Voltage Divider

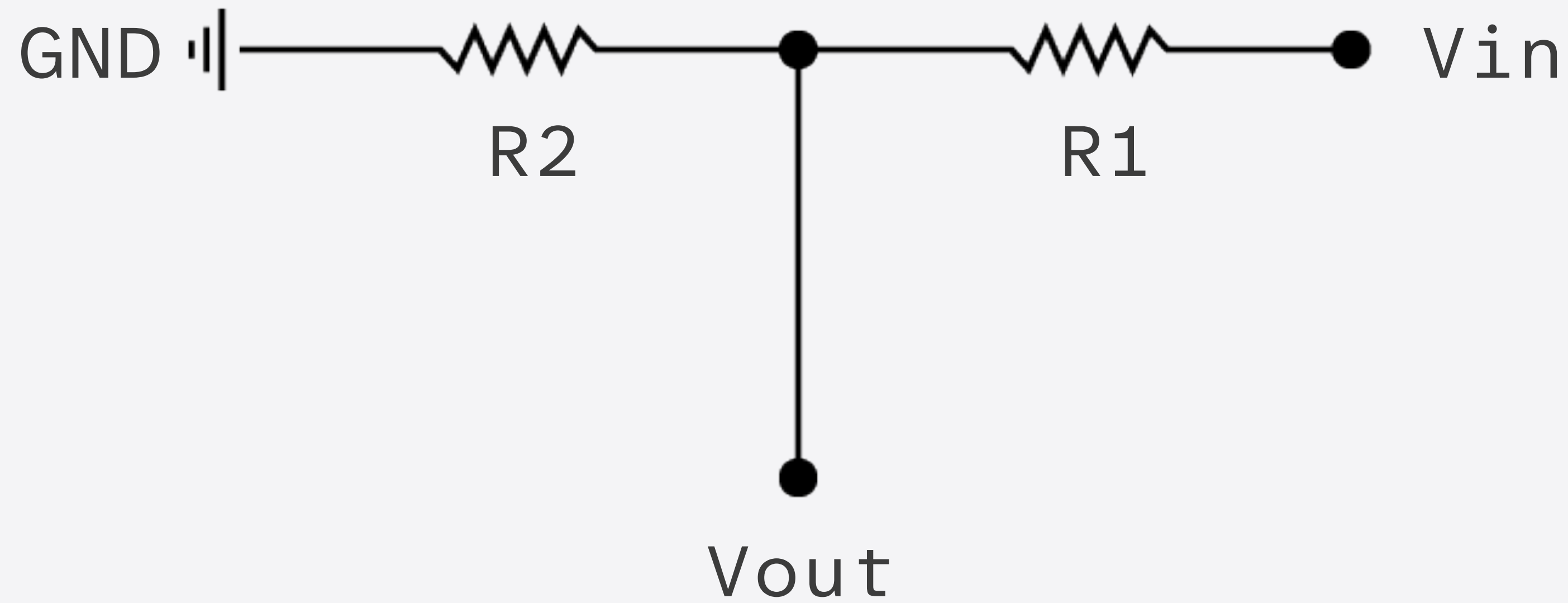


The result comes on V_{out} .

Voltage Divider

$$V_{out} = V_{in} \cdot \frac{R_2}{R_1 + R_2}$$


This equation lets you calculate the values.

Voltage Divider

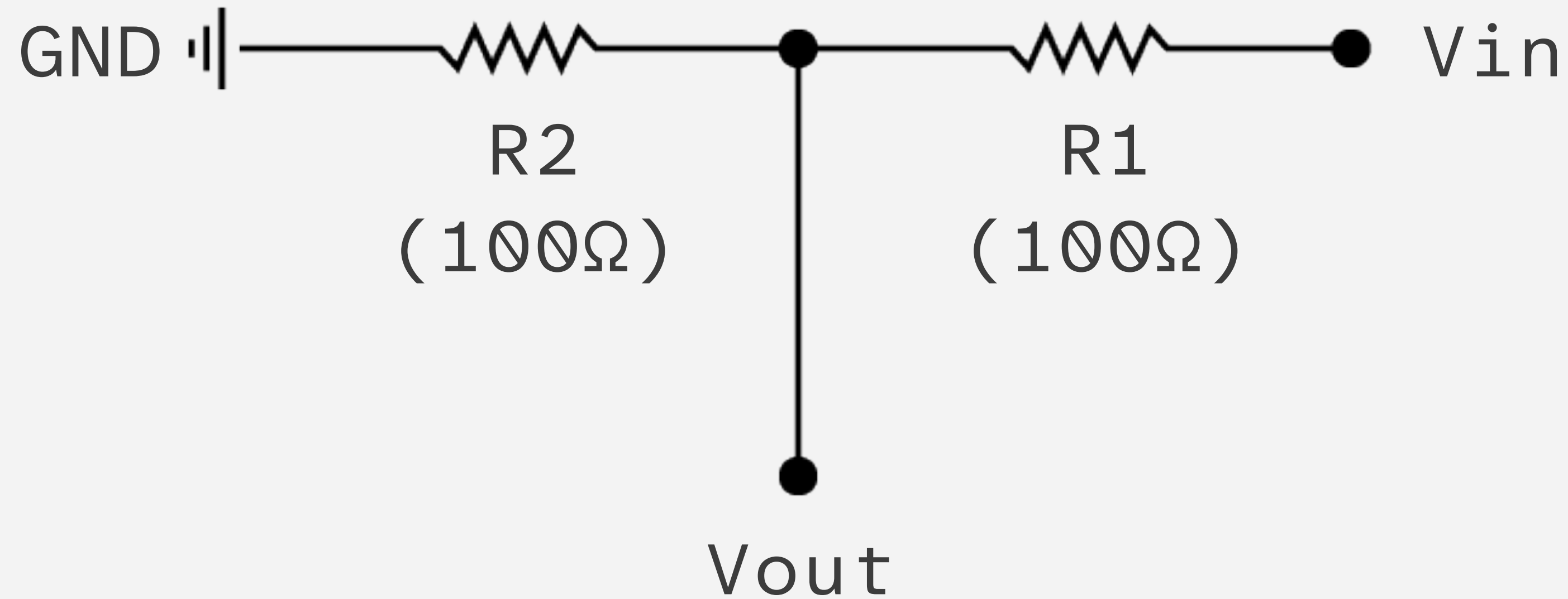


If $R1$ and $R2$ are equal
Then the output voltage is half
that of the input.

Voltage Divider

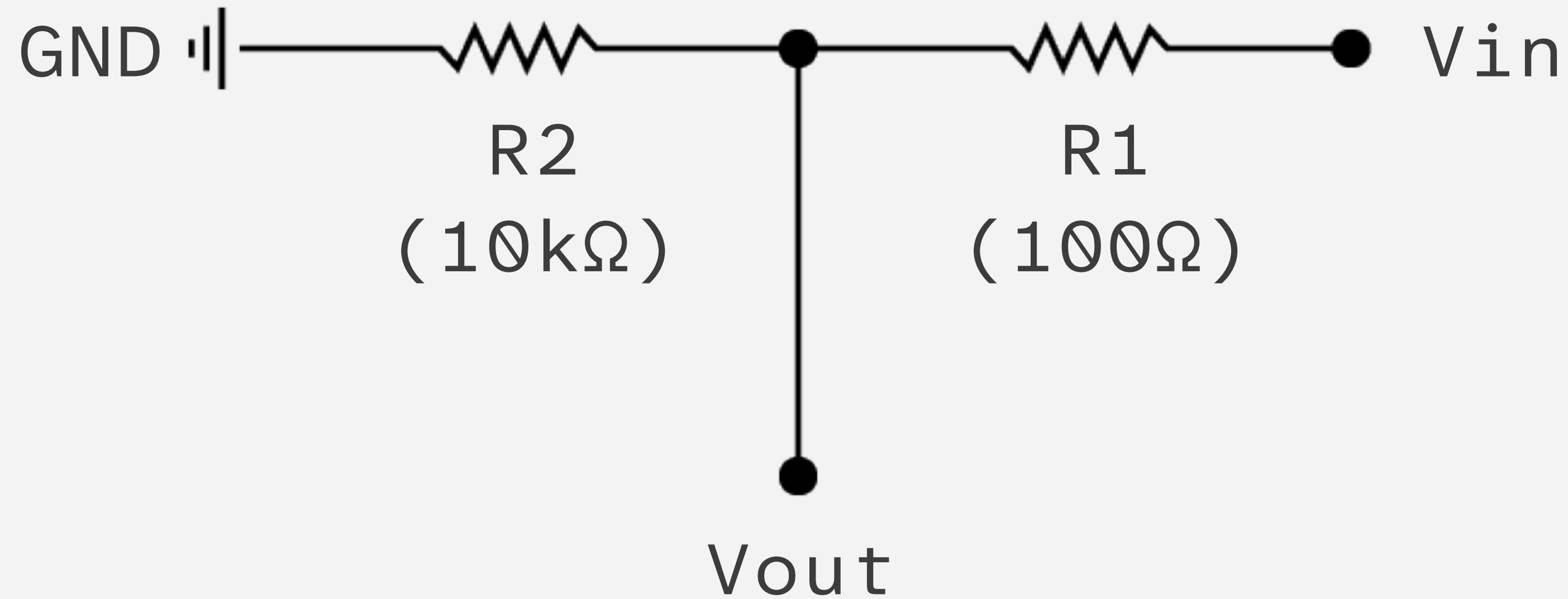



If R_2 is much larger than R_1
Then the output voltage will be
very close to the input.

Voltage Divider

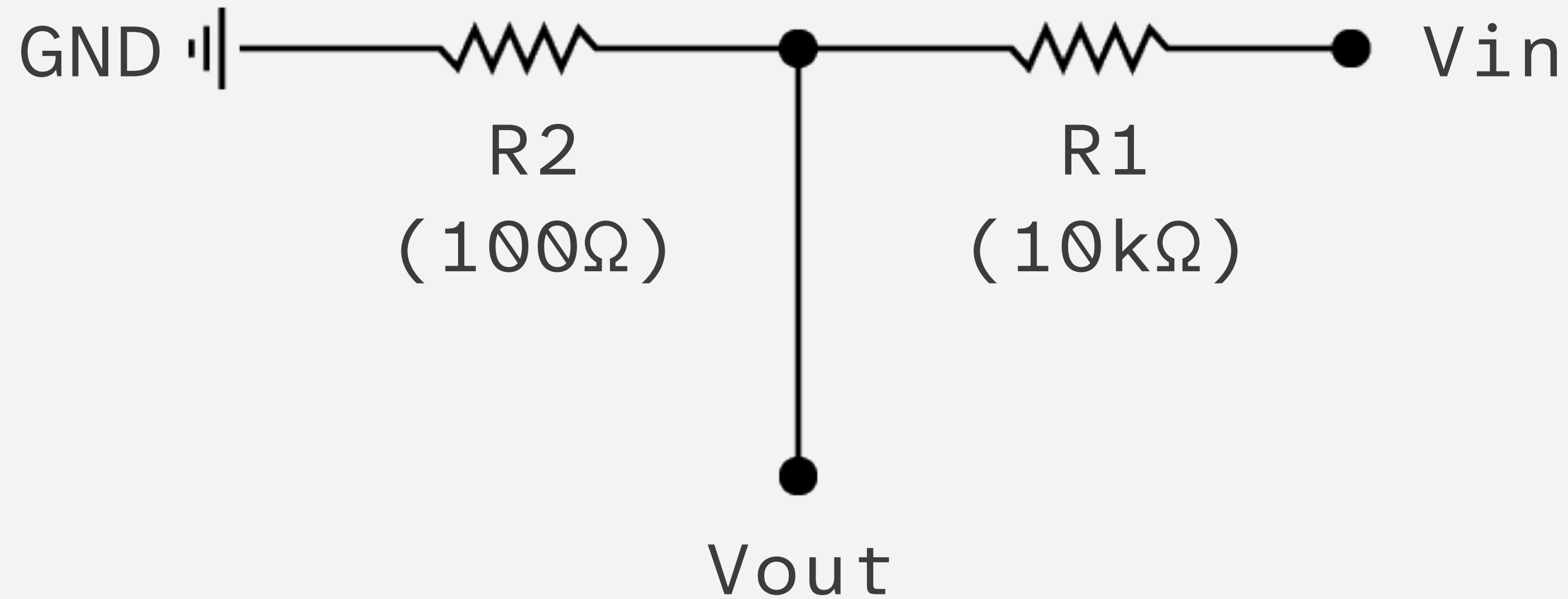


If R_2 is much smaller than R_1
Then output voltage will be tiny
compared to the input.


Voltage Divider

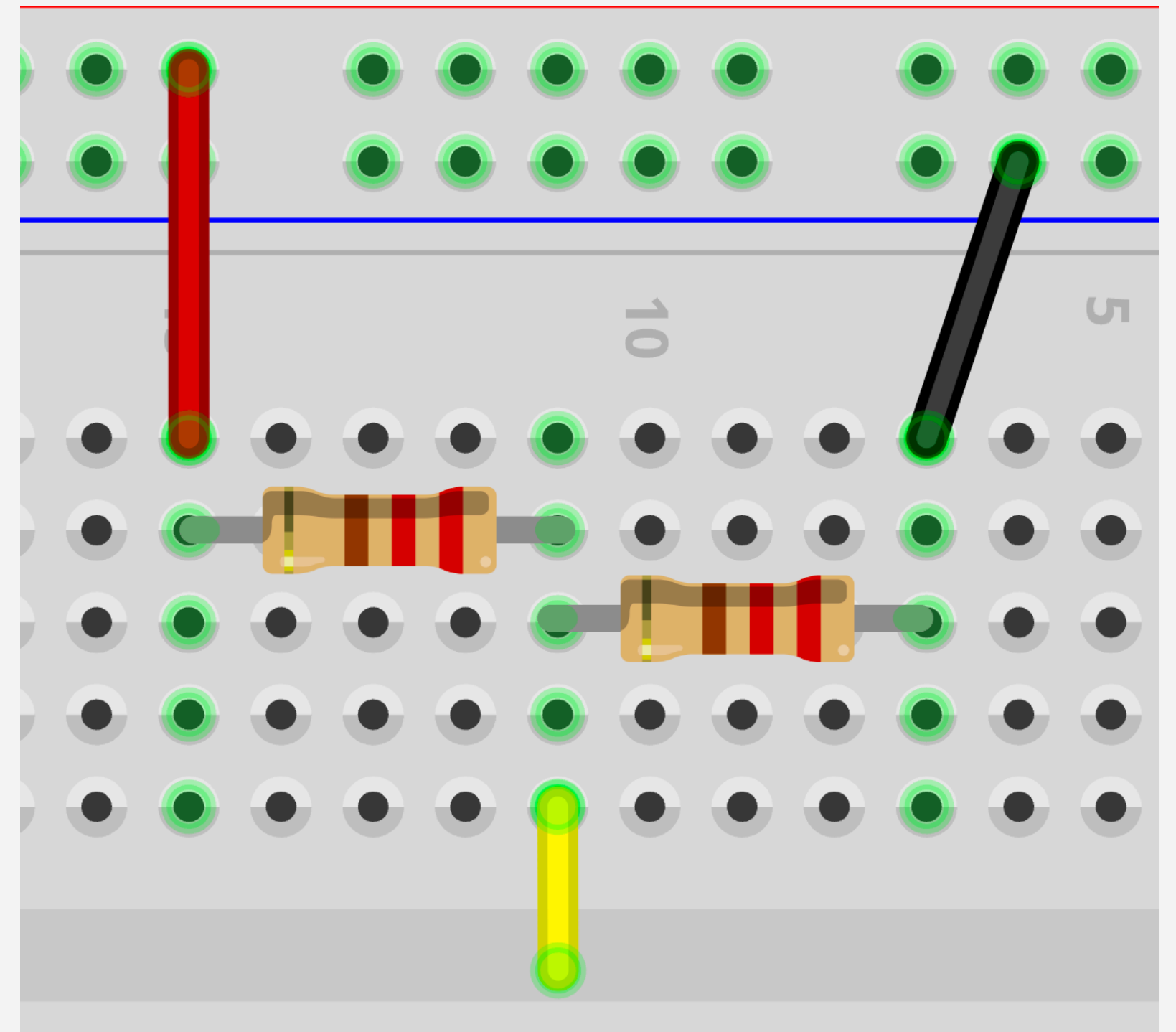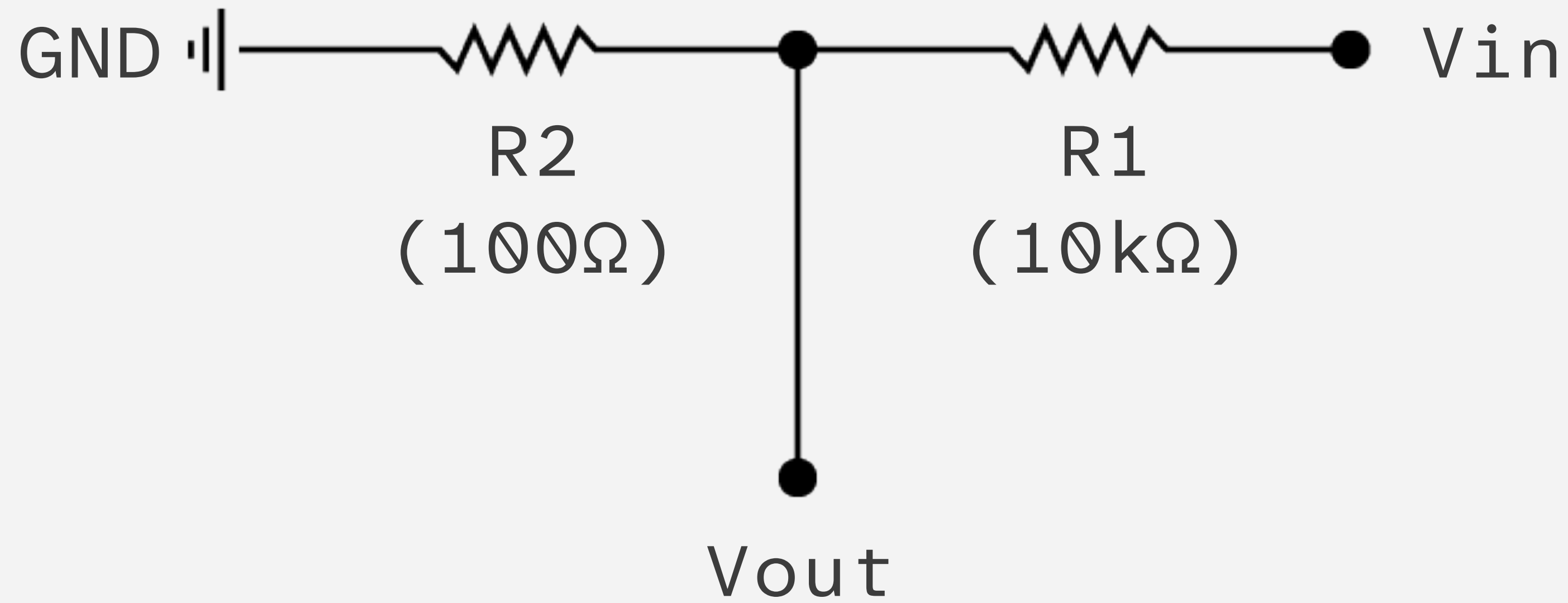

Voltage Divider + LDR*

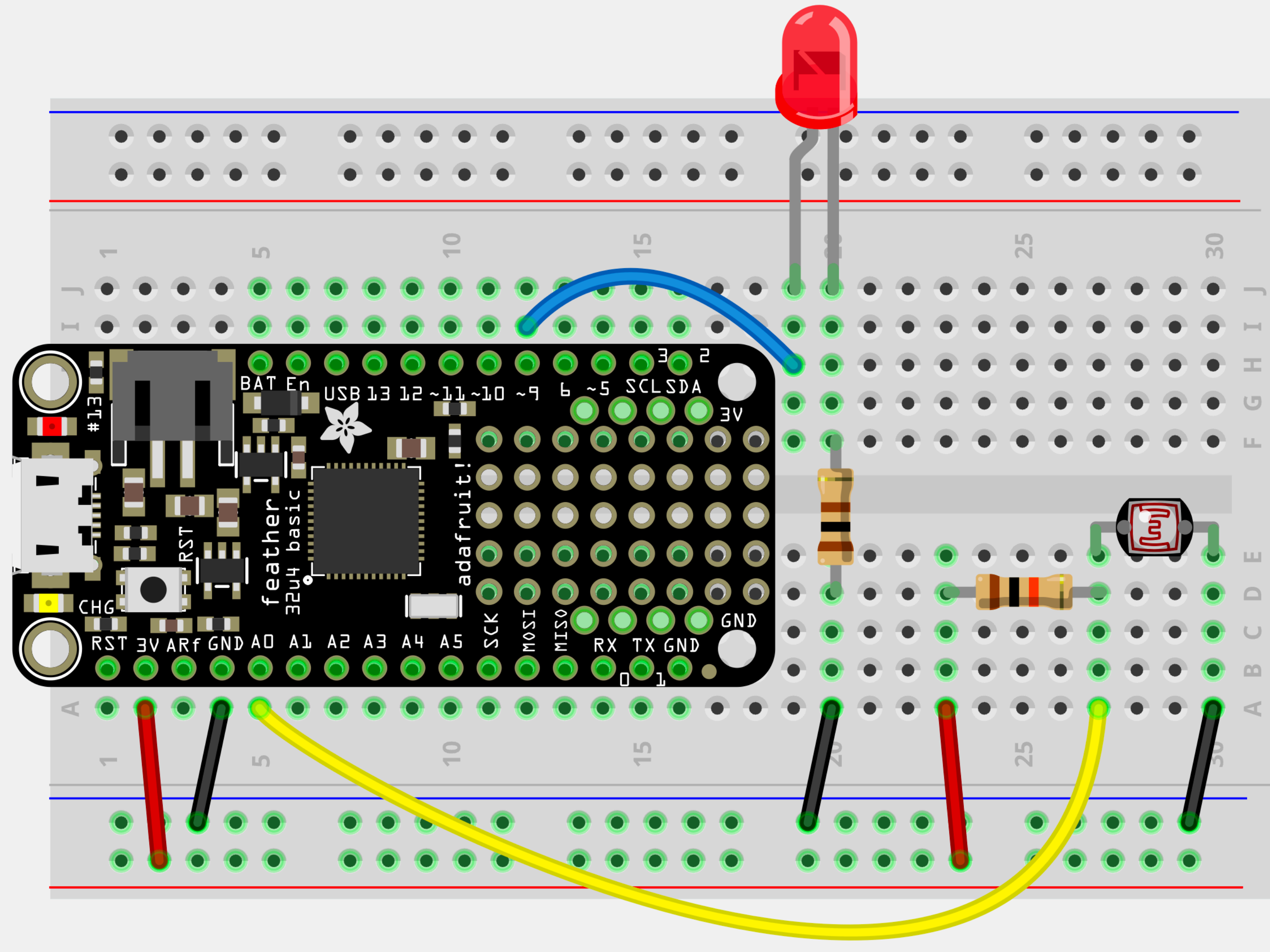

* Light Dependent Resistor

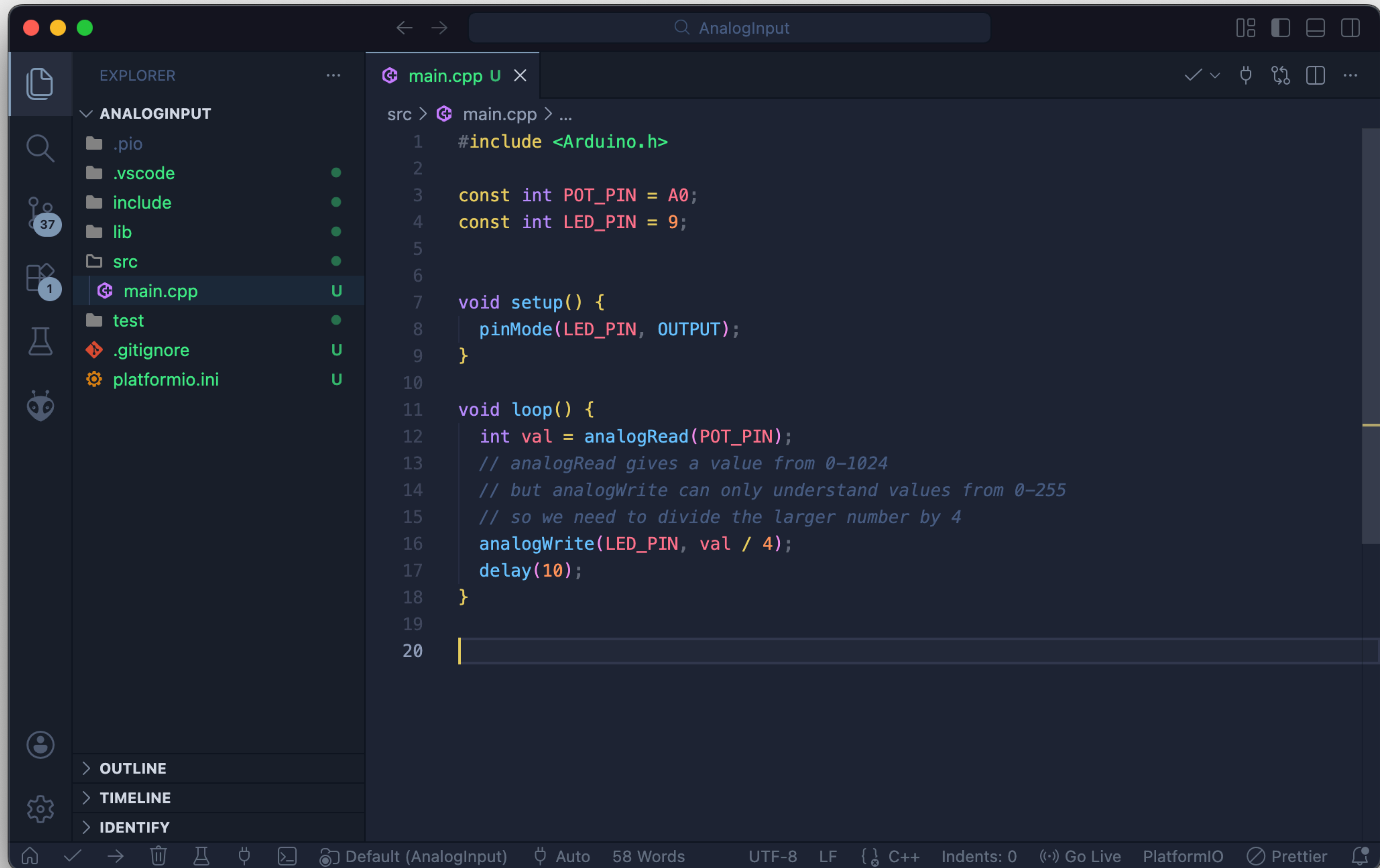


Voltage Divider + LDR*

Light Level	R ₂ (Sensor)	R ₁ (Fixed)	R ₂ /(R ₁ +R ₂)	V _{out}	Value from analogRead
Bright	300Ω	10kΩ	0.029	0.096 V	~30
Dim	7kΩ	10kΩ	0.411	1.35 V	~420
Dark	40kΩ	10kΩ	0.800	2.64 V	~819

* Light Dependent Resistor

Voltage Divider + FSR*

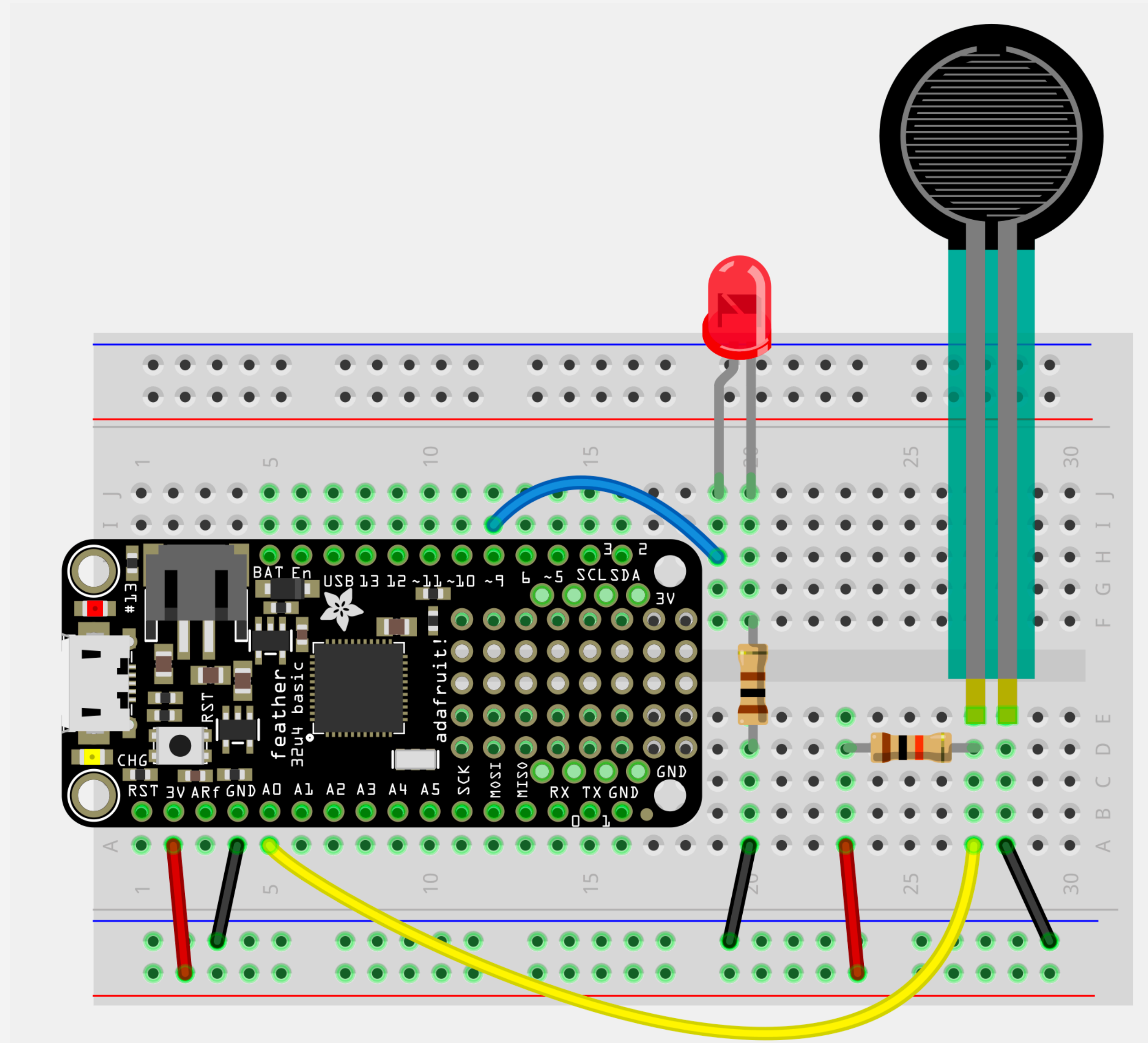

* Force Sensing Resistor

