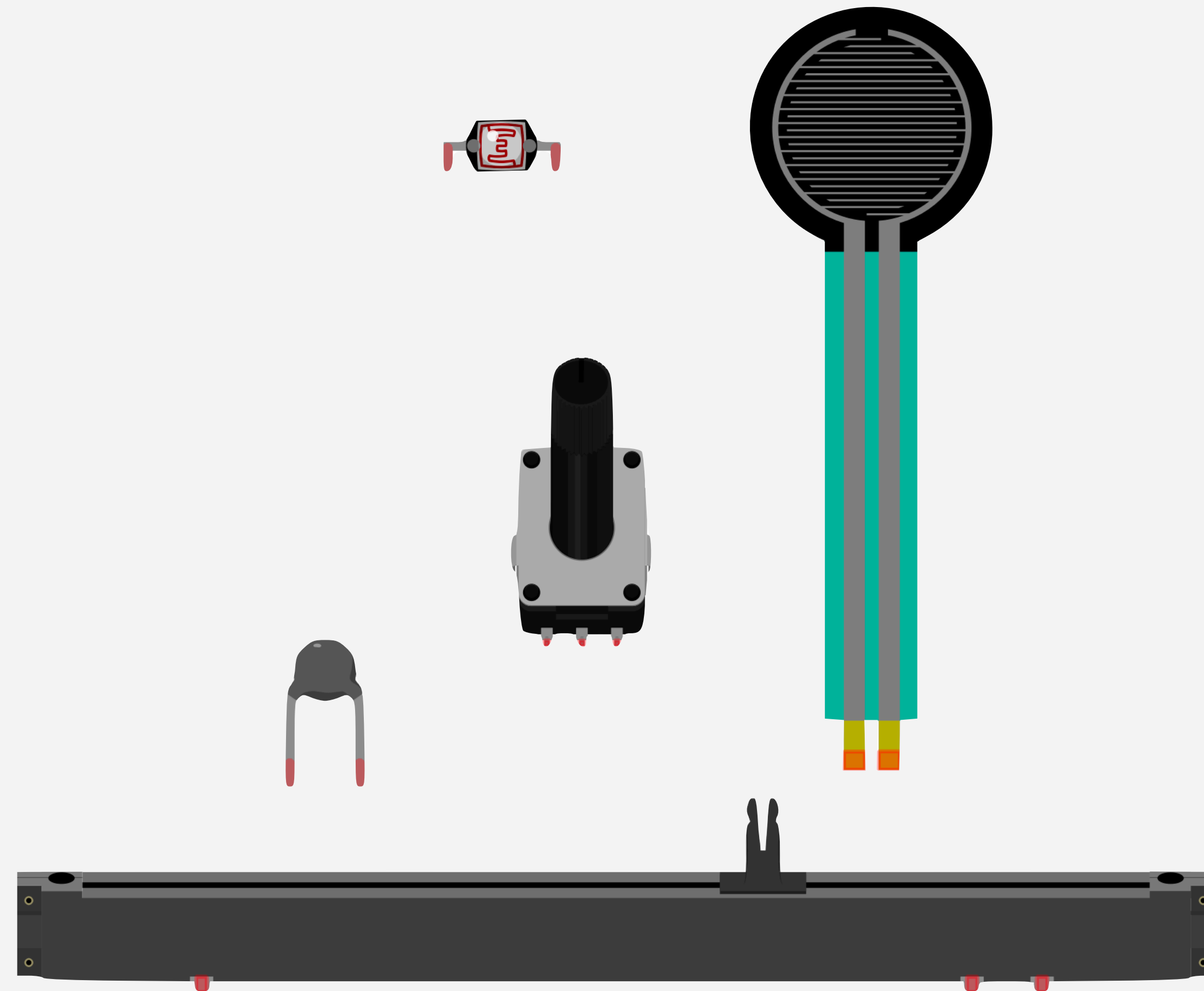


# ANALOG INPUT





**Knobs, Sliders, Temperature,  
Light, & more!**

# Analog Input

An analog input is any device that can create or transmit a range of values beyond just on/off.



# Using Analog Inputs with the Arduino

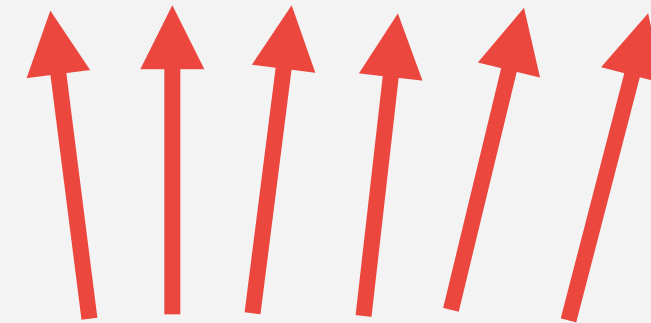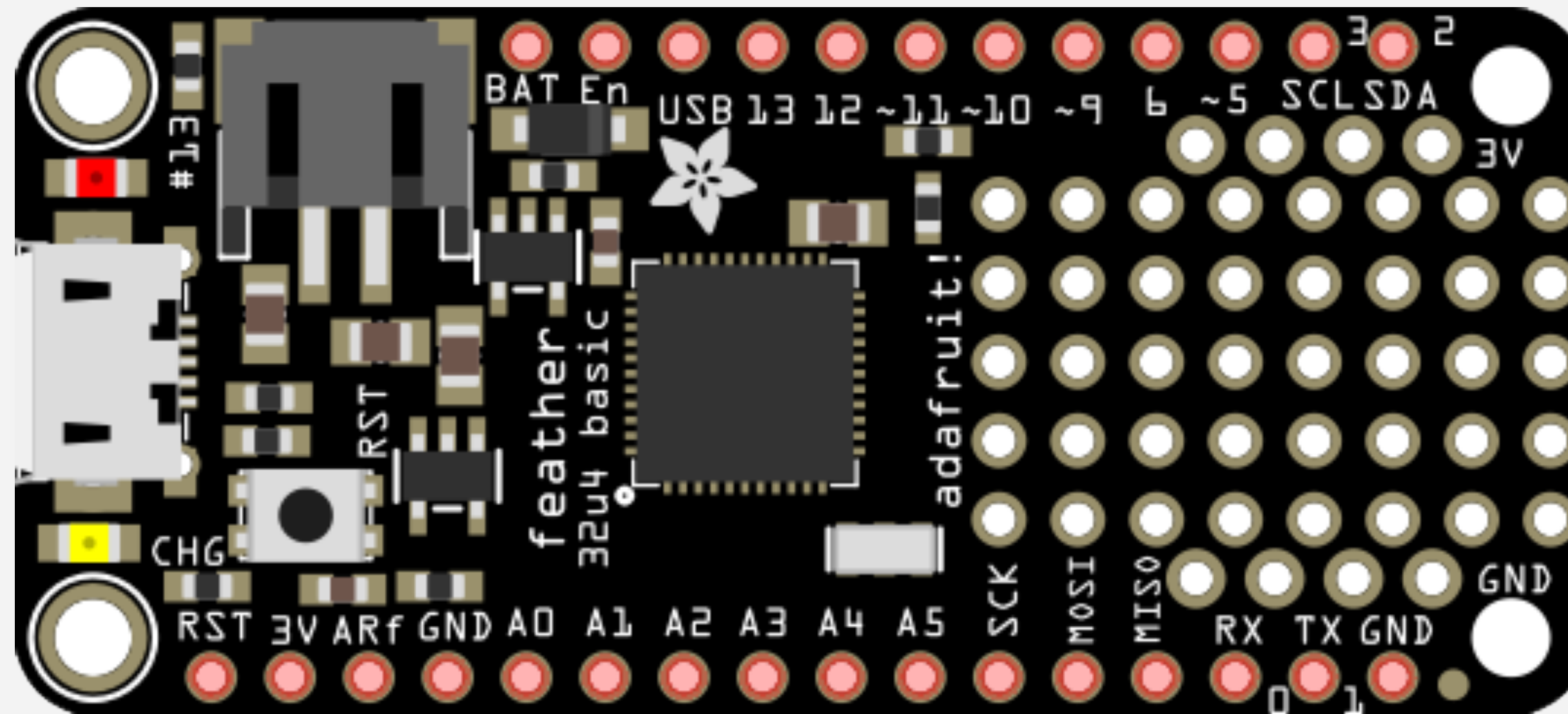

**Analog Input Pins**

# Analog Input

The inputs on the Arduino read voltage.


All inputs need to be thought of in terms of voltage differentials.


Unlike digital inputs, analog inputs convert differences in voltage levels into a number from 0-1024



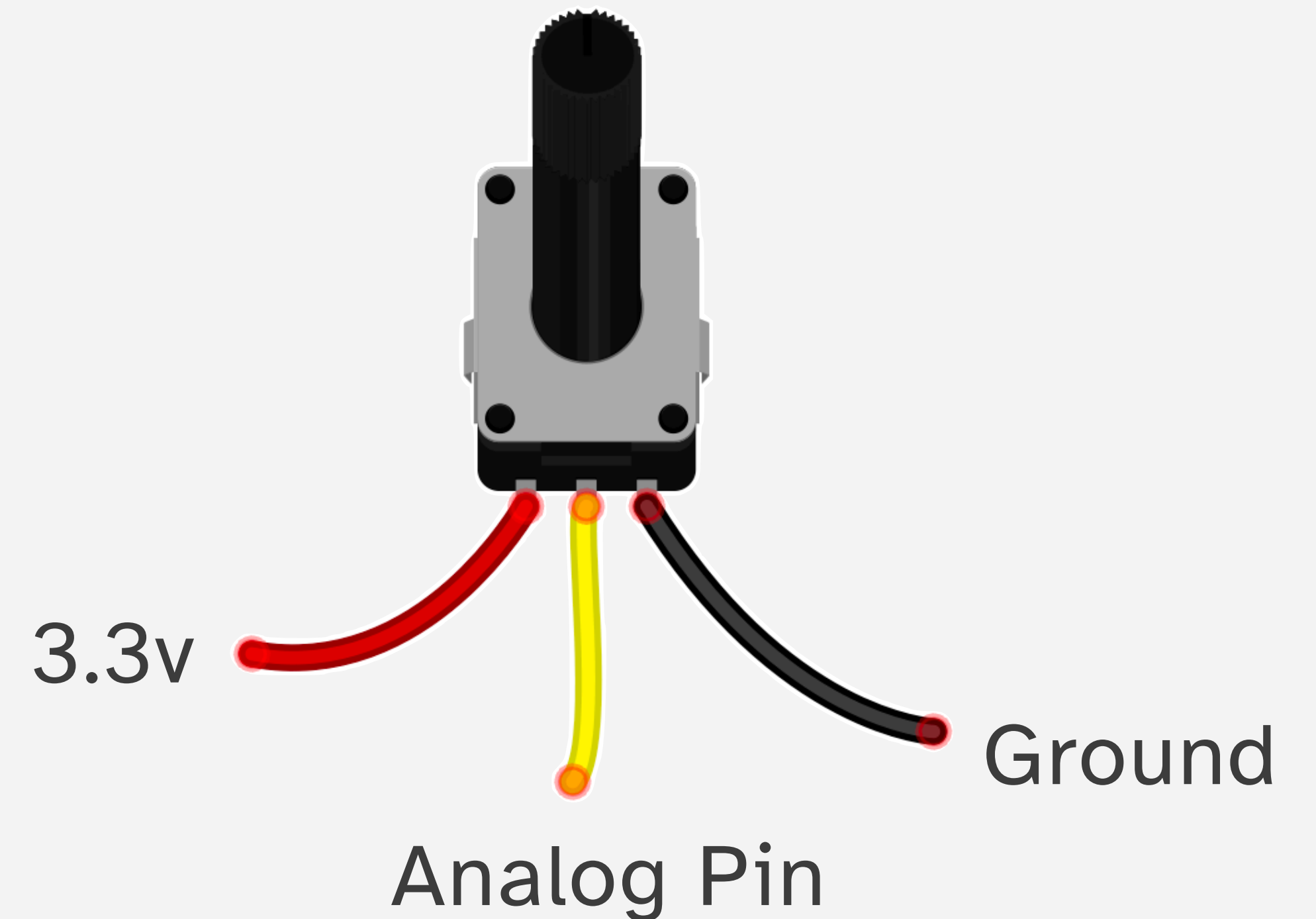
# Analog Input


The potentiometer is the easiest analog input to use. It has three connections.



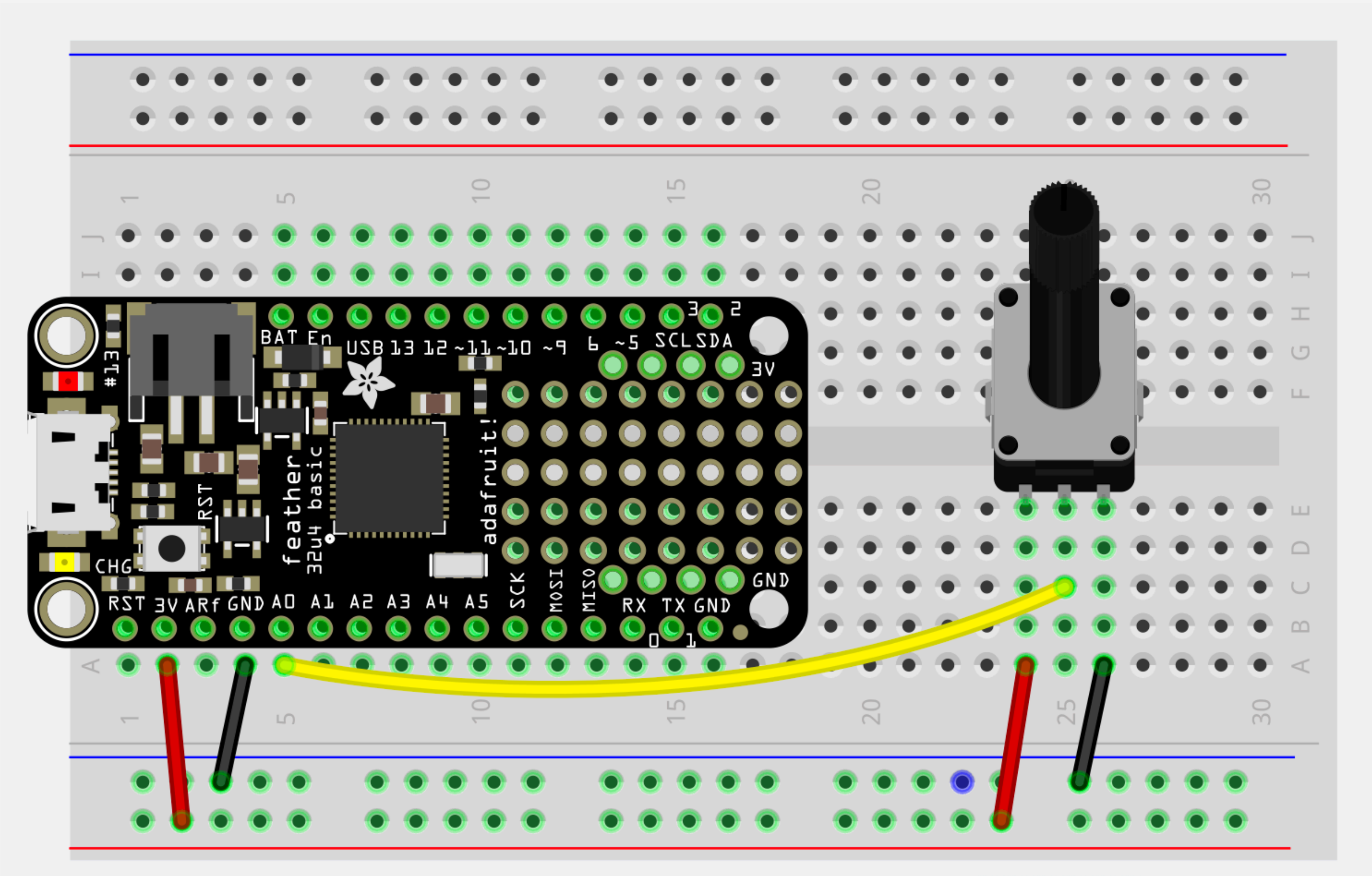




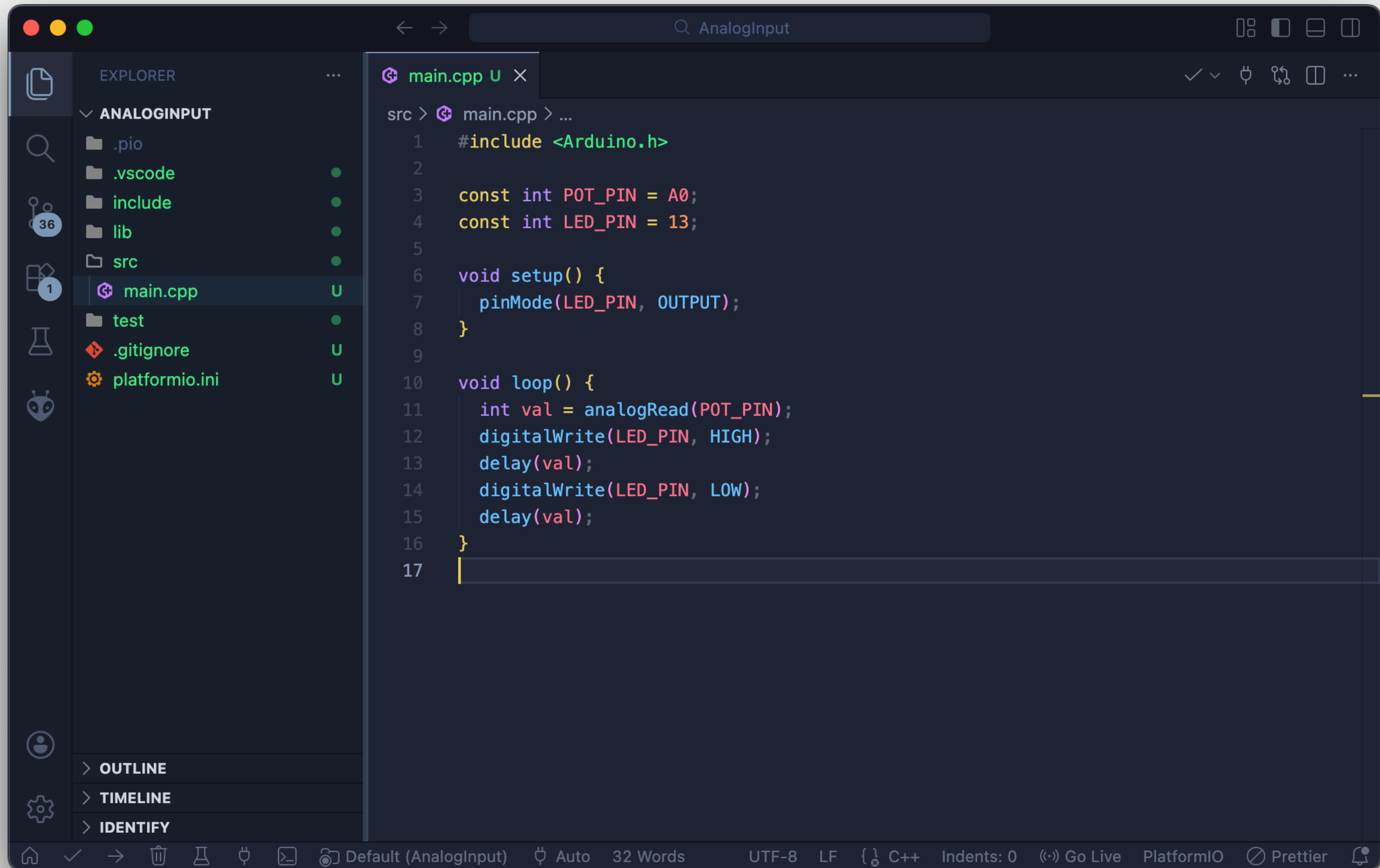

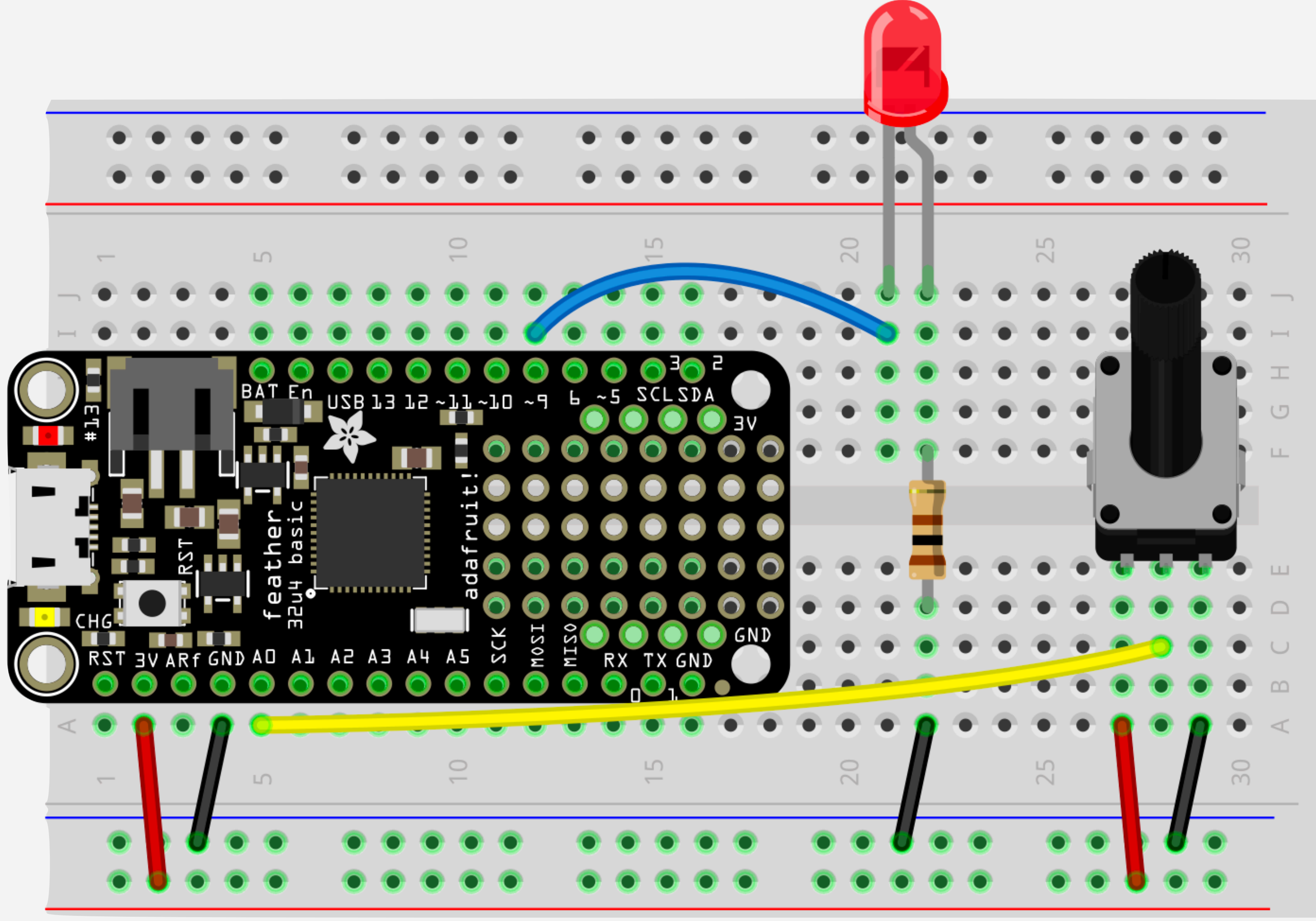




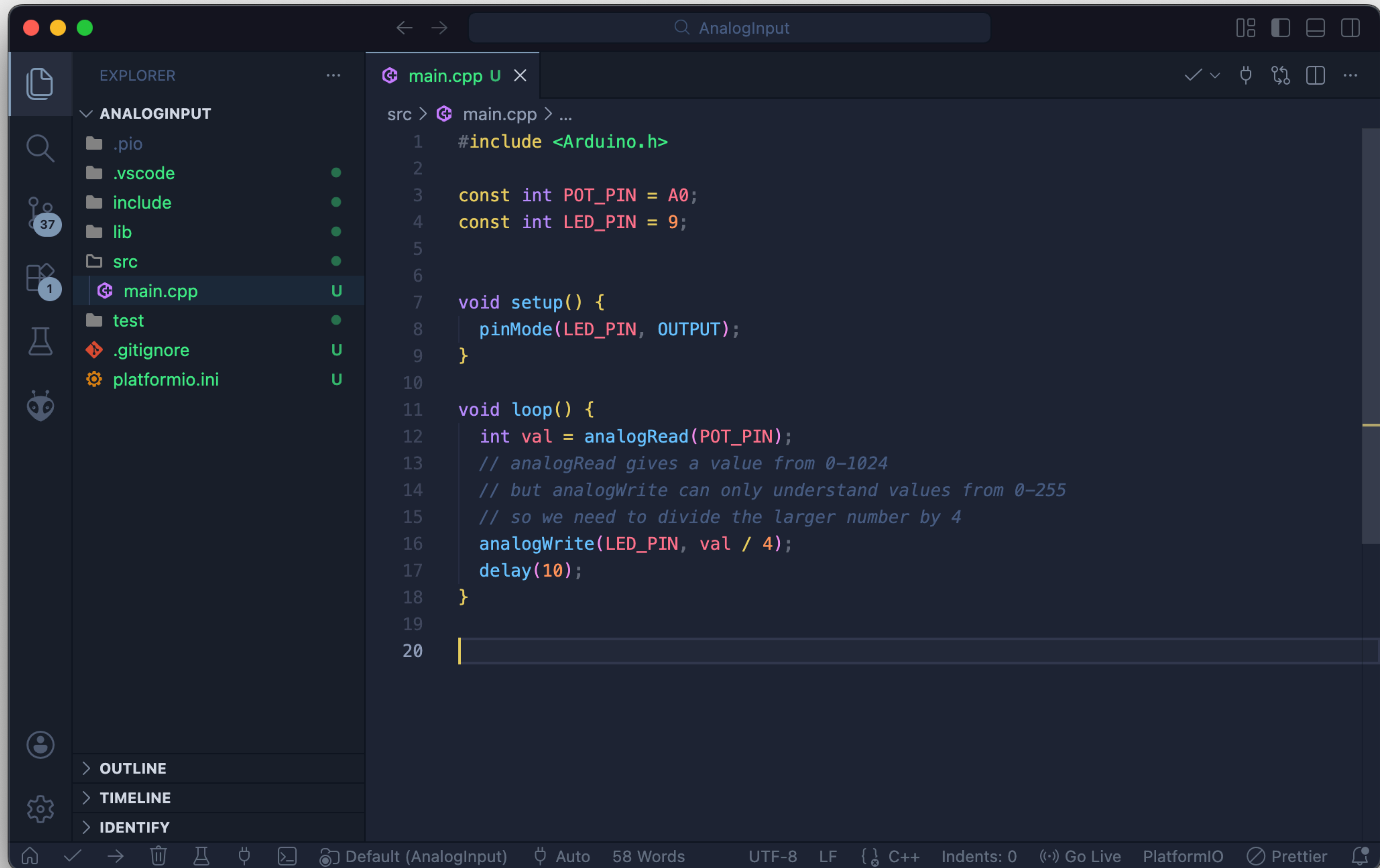

# **VOLTAGE DIVIDERS**


# Voltage Divider

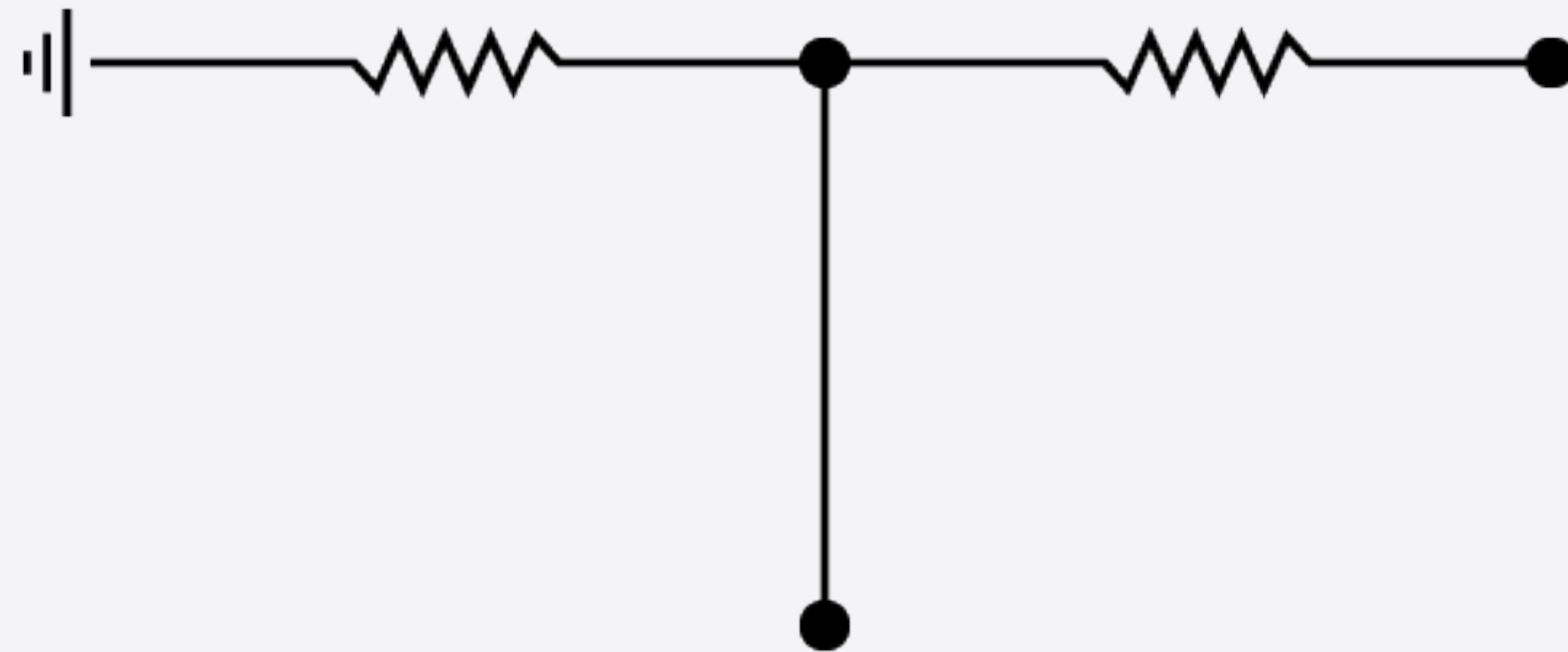

The Voltage Divider is a simple circuit that lets you convert a change in resistance into a change in voltage.




# Voltage Divider

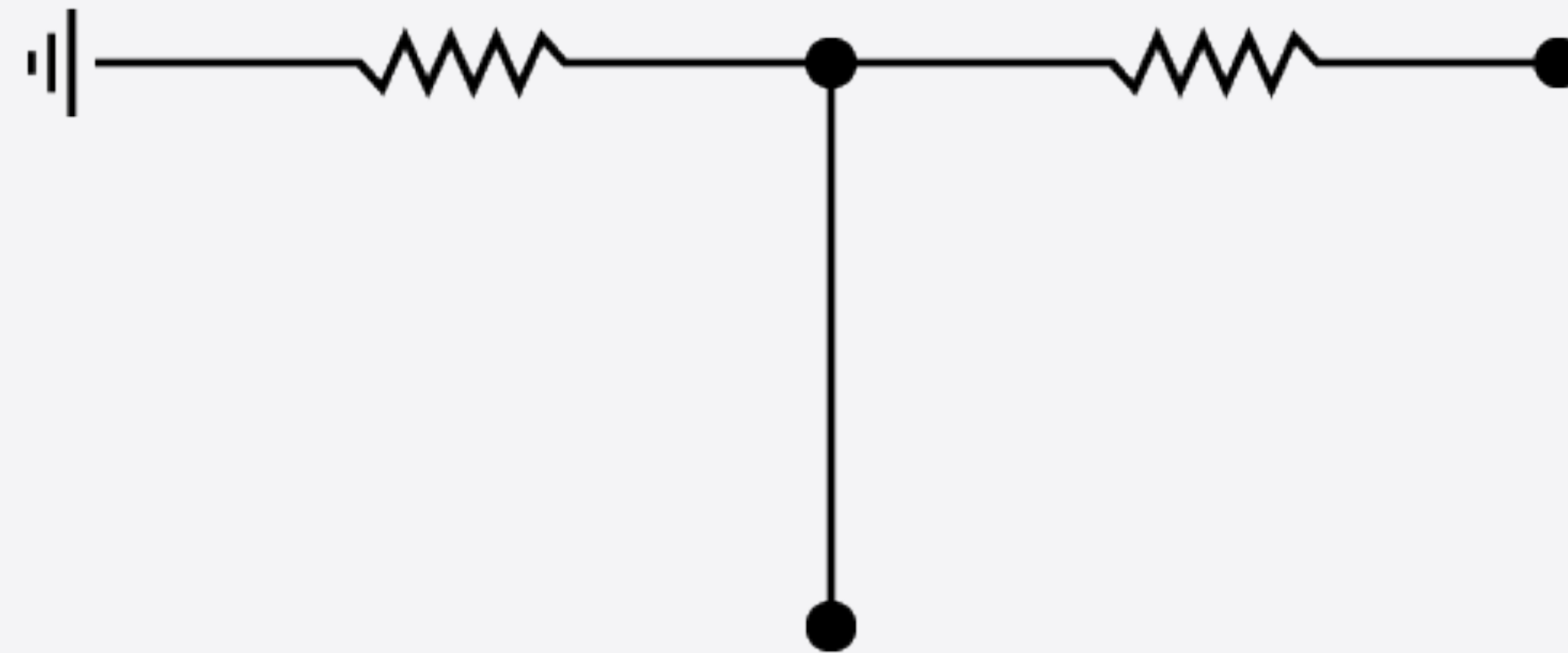

This is useful because there are a number of sensors that change resistance, but the Arduino can only sense changes in voltage.


# Voltage Divider

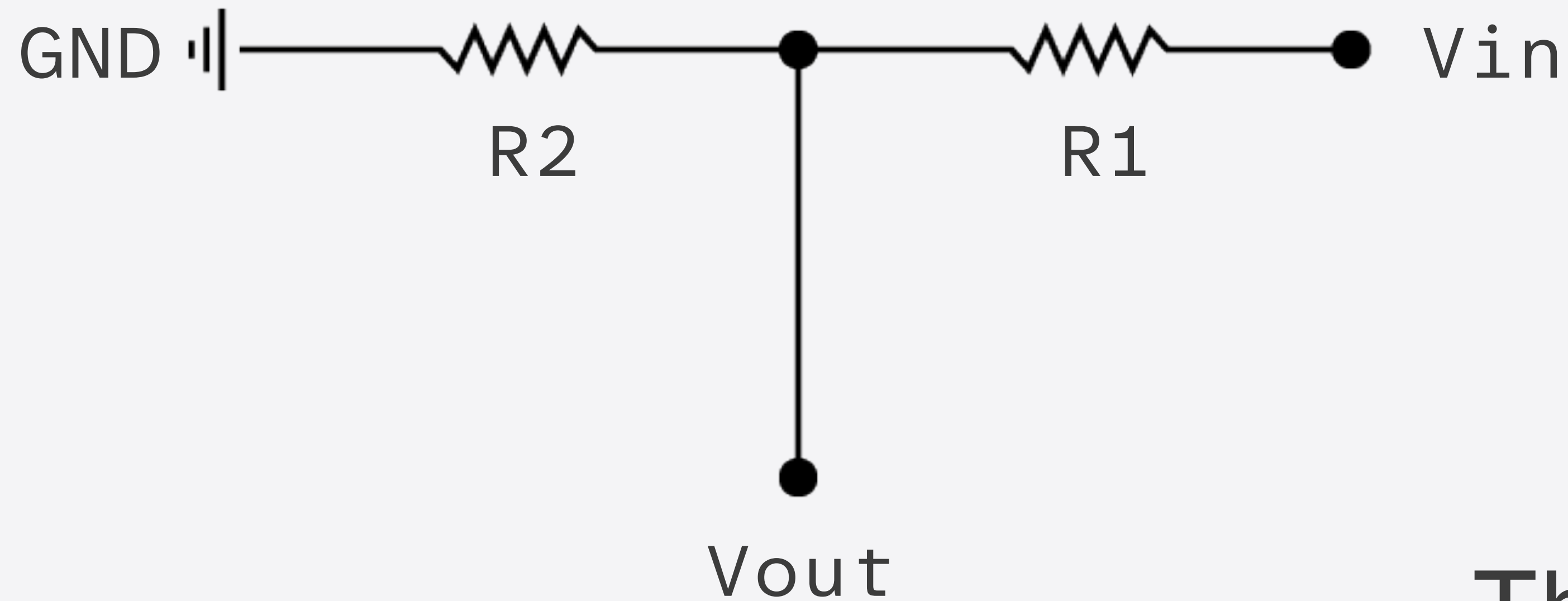

The resistor closest to ground is called R2.

The resistor closest to the input voltage ( $V_{in}$ ) is called R1.

# Voltage Divider

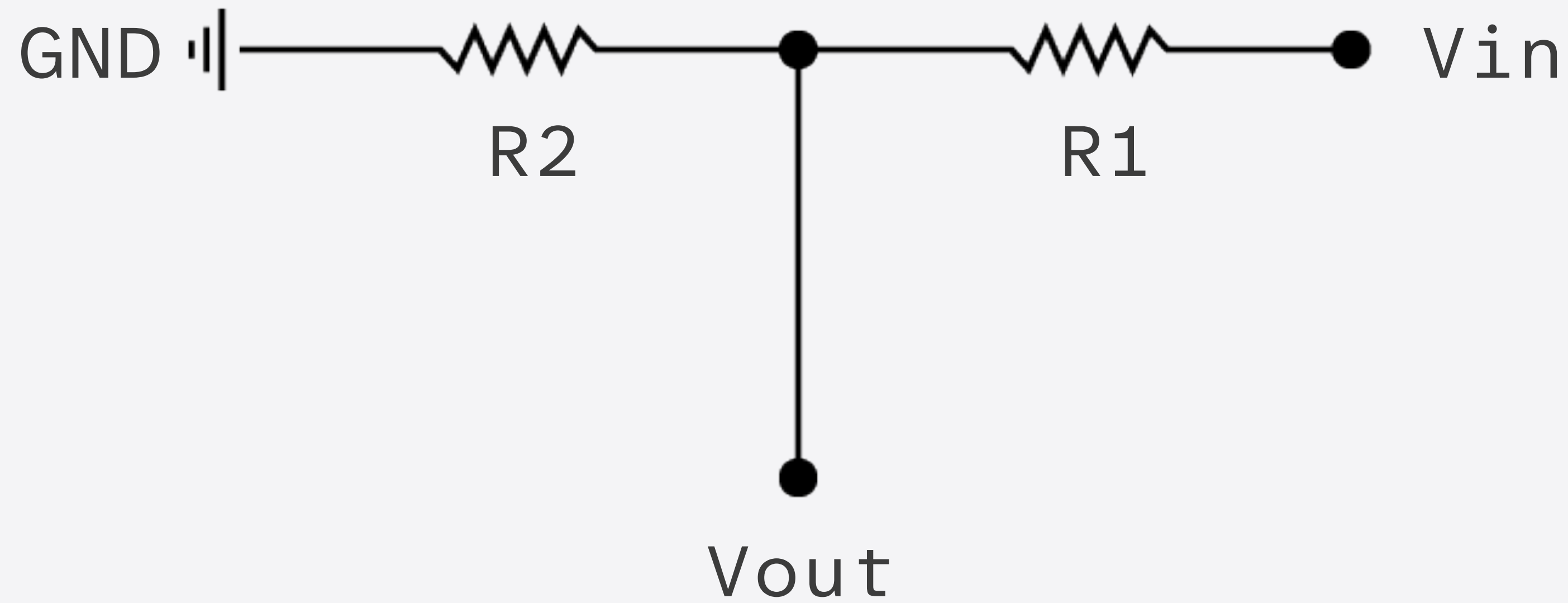

The result comes on  $V_{out}$ .




# Voltage Divider

$$V_{out} = V_{in} \cdot \frac{R_2}{R_1 + R_2}$$


This equation lets you calculate the values.

# Voltage Divider

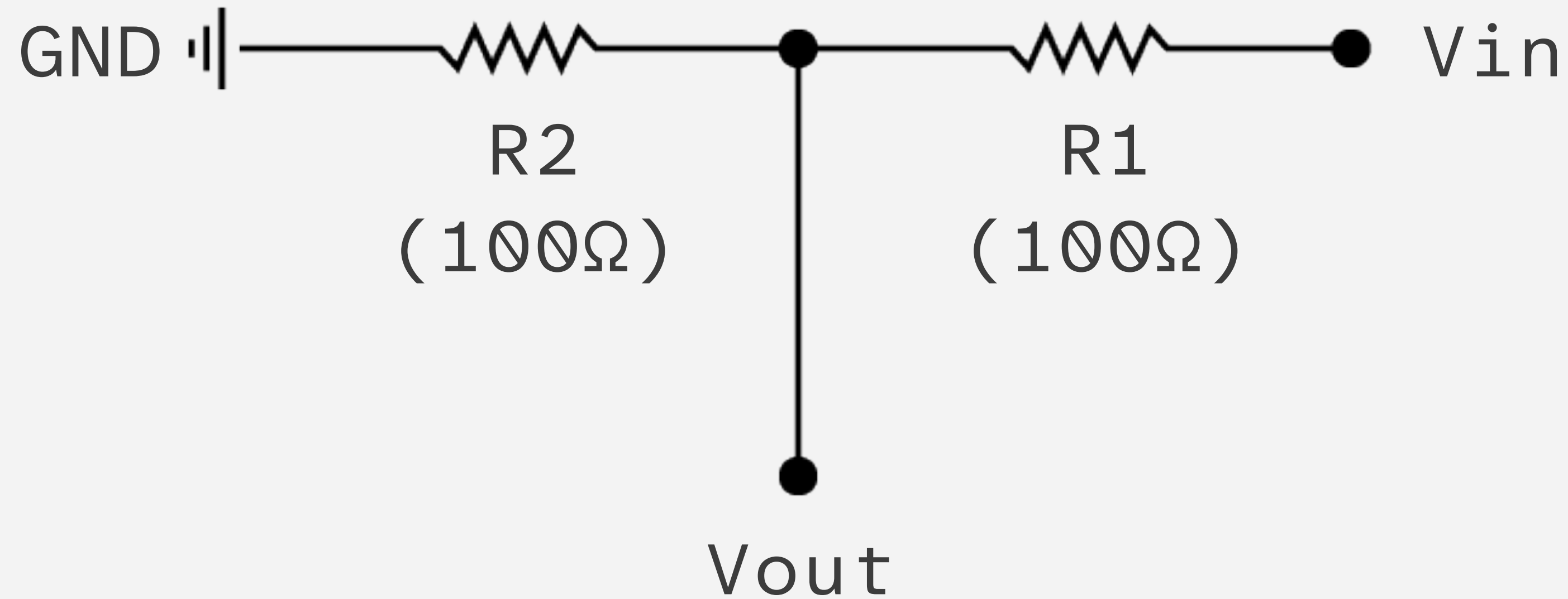

If  $R1$  and  $R2$  are equal  
Then the output voltage is half  
that of the input.


# Voltage Divider

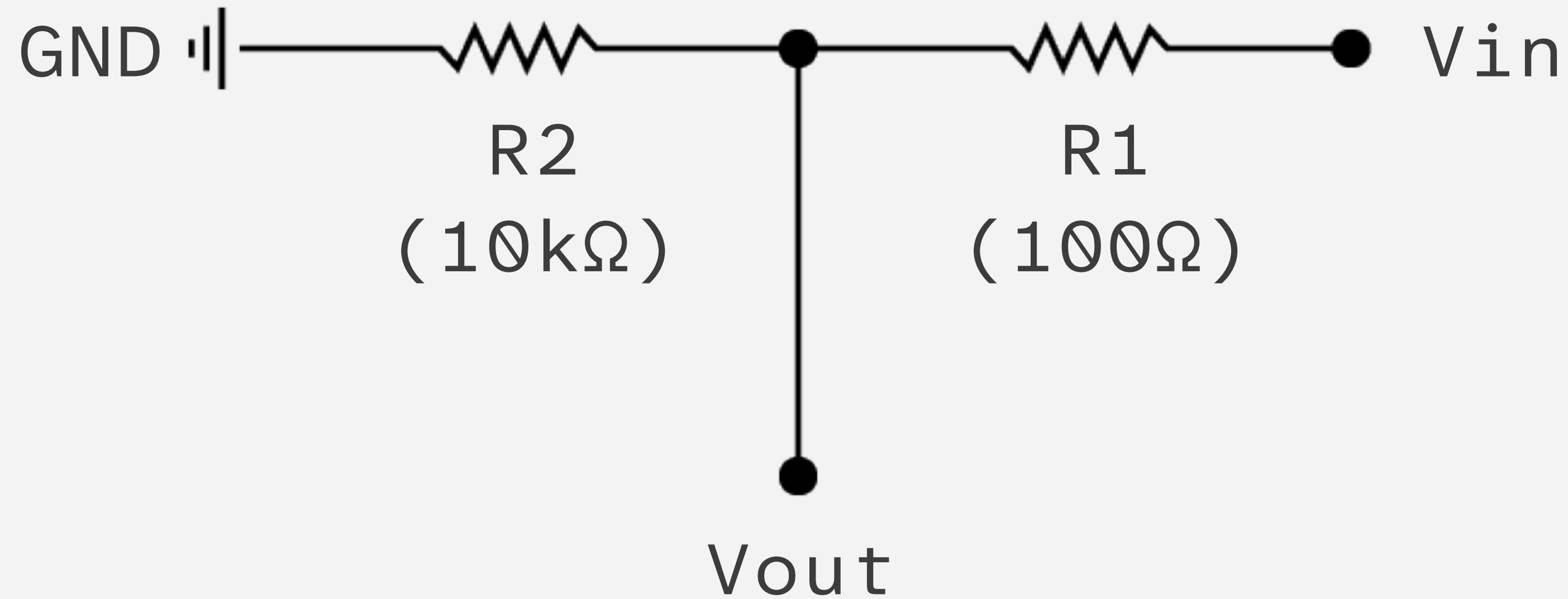

If  $R_2$  is much larger than  $R_1$   
Then the output voltage will be  
very close to the input.




# Voltage Divider

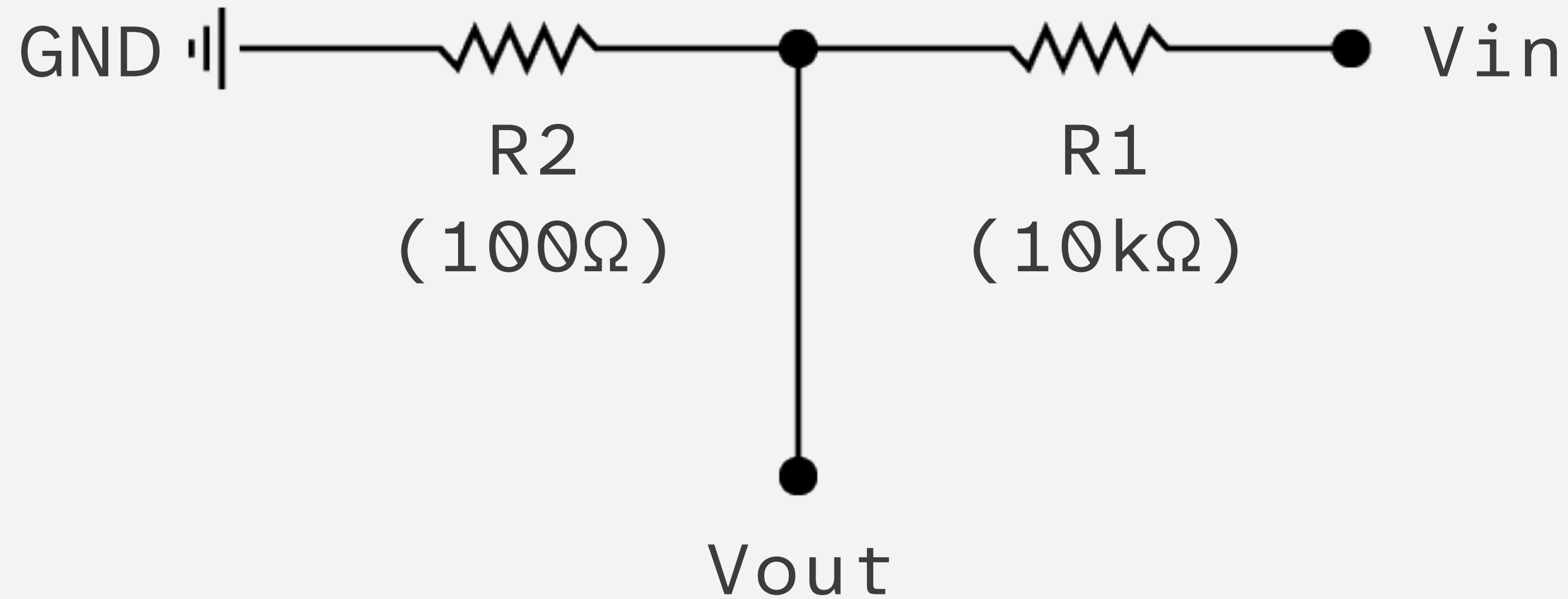


If  $R2$  is much smaller than  $R1$   
Then output voltage will be tiny  
compared to the input.

# Voltage Divider + LDR\*

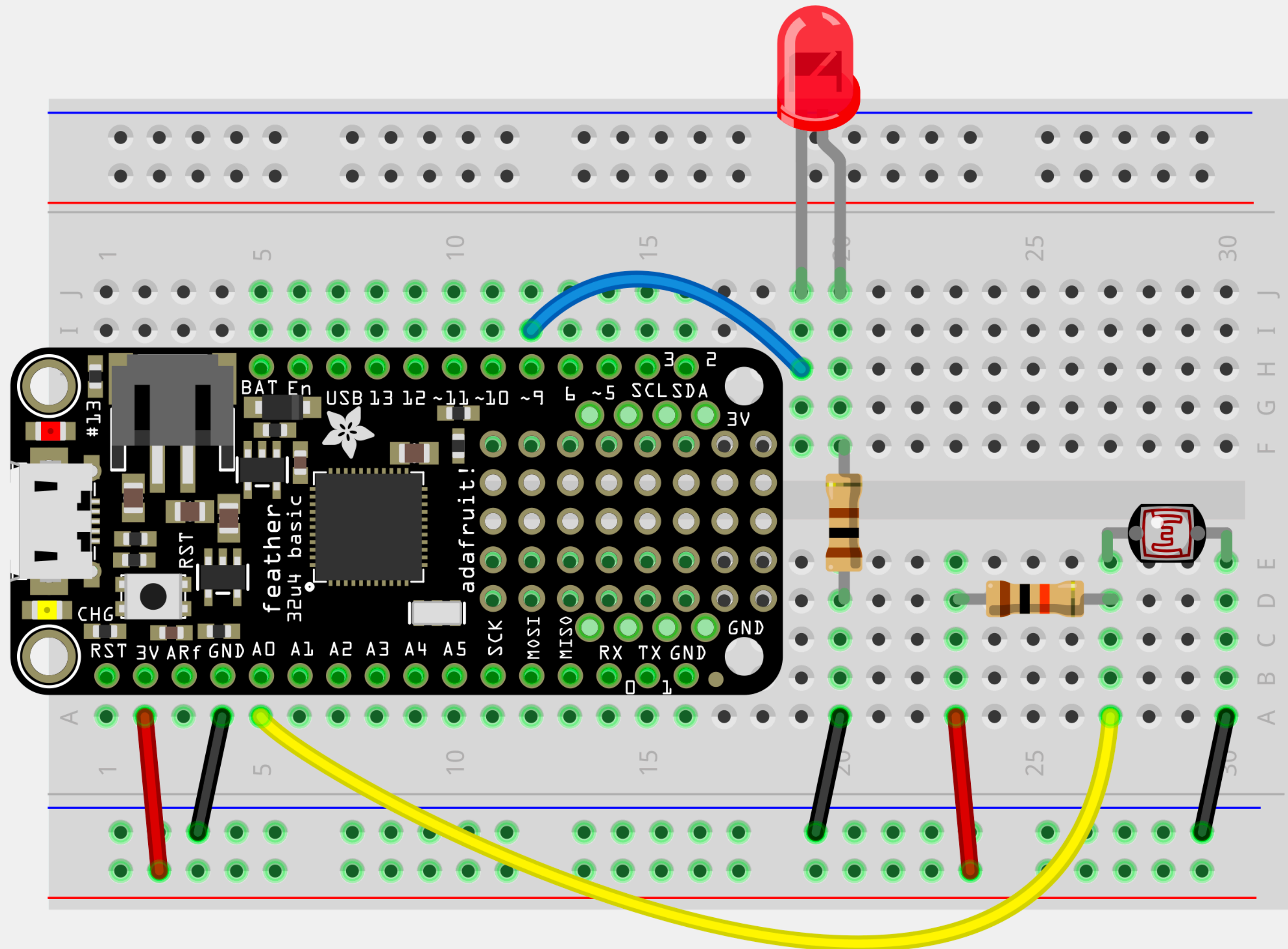

\* Light Dependent Resistor

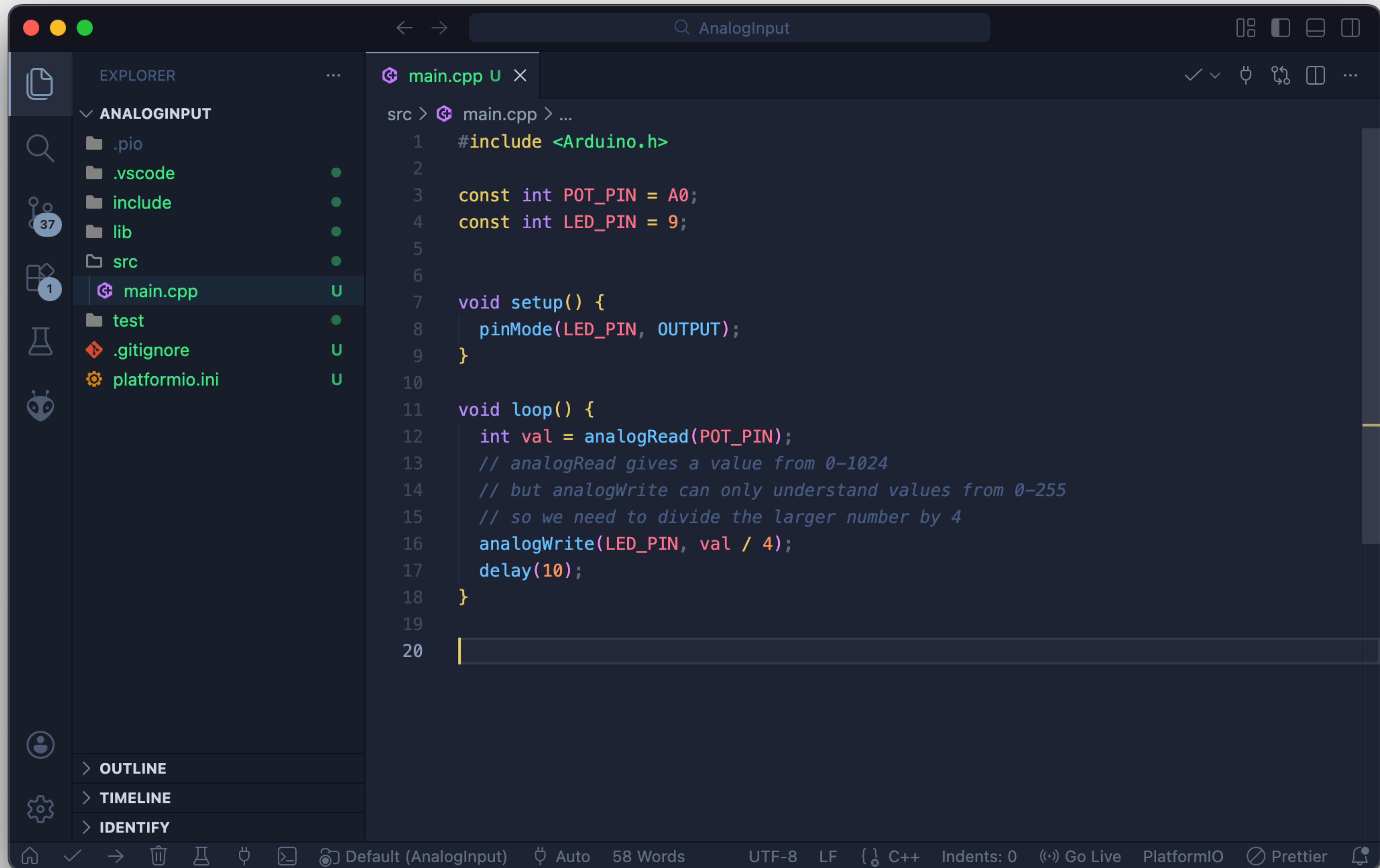




# Voltage Divider + LDR\*

| Light Level | R <sub>2</sub> (Sensor) | R <sub>1</sub> (Fixed) | R <sub>2</sub> /(R <sub>1</sub> +R <sub>2</sub> ) | V <sub>out</sub> | Value from analogRead |
|-------------|-------------------------|------------------------|---------------------------------------------------|------------------|-----------------------|
| Bright      | 300Ω                    | 10kΩ                   | 0.029                                             | 0.096 V          | ~30                   |
| Dim         | 7kΩ                     | 10kΩ                   | 0.411                                             | 1.35 V           | ~420                  |
| Dark        | 40kΩ                    | 10kΩ                   | 0.800                                             | 2.64 V           | ~819                  |

\* Light Dependent Resistor

# Voltage Divider + FSR\*

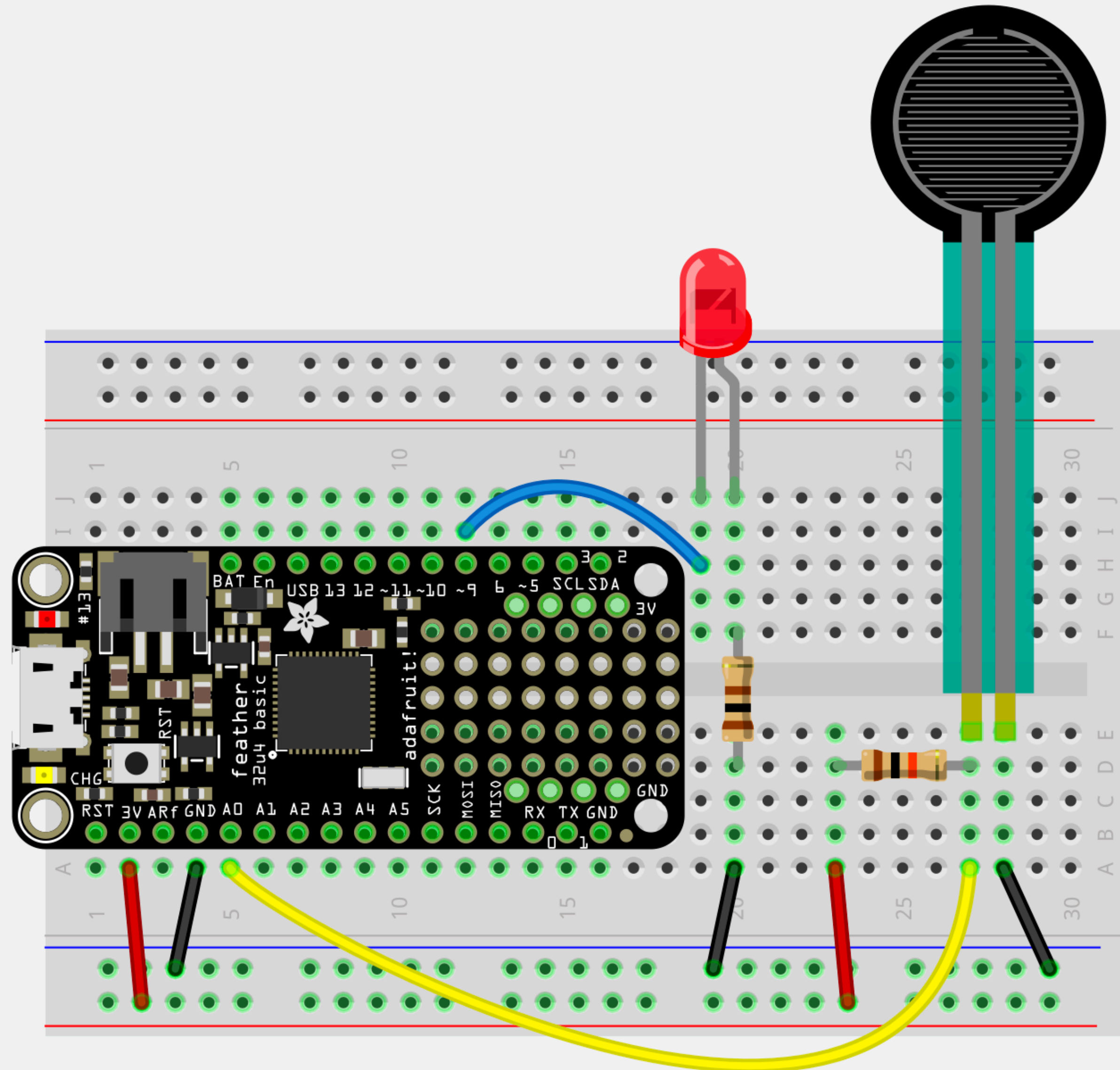

\* Force Sensing Resistor

