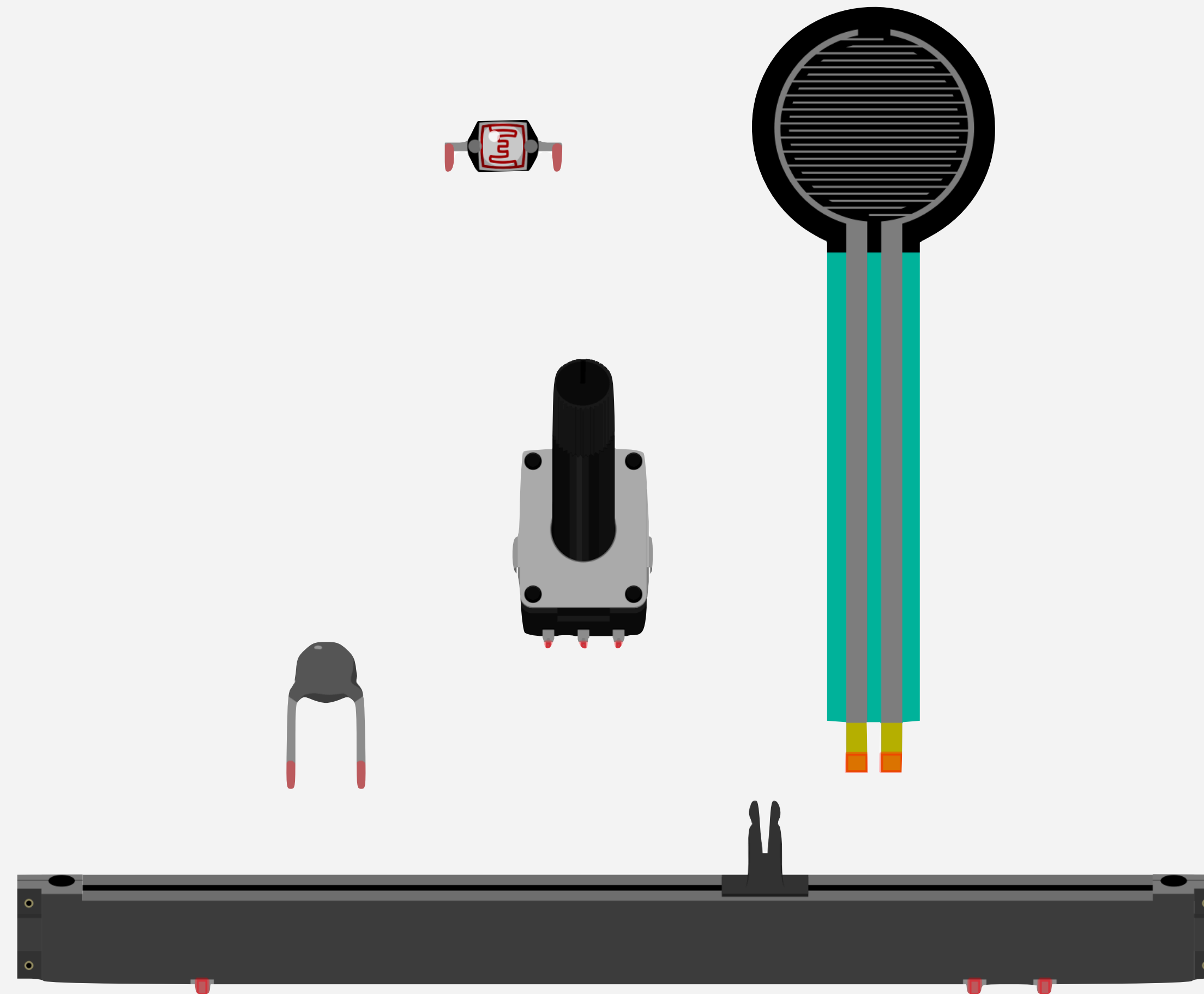


# ANALOG INPUT




**Knobs, Sliders, Temperature,  
Light, & more!**

# Analog Input

An analog input is any device that can create or transmit a range of values beyond just on/off.

# Using Analog Inputs with the Arduino

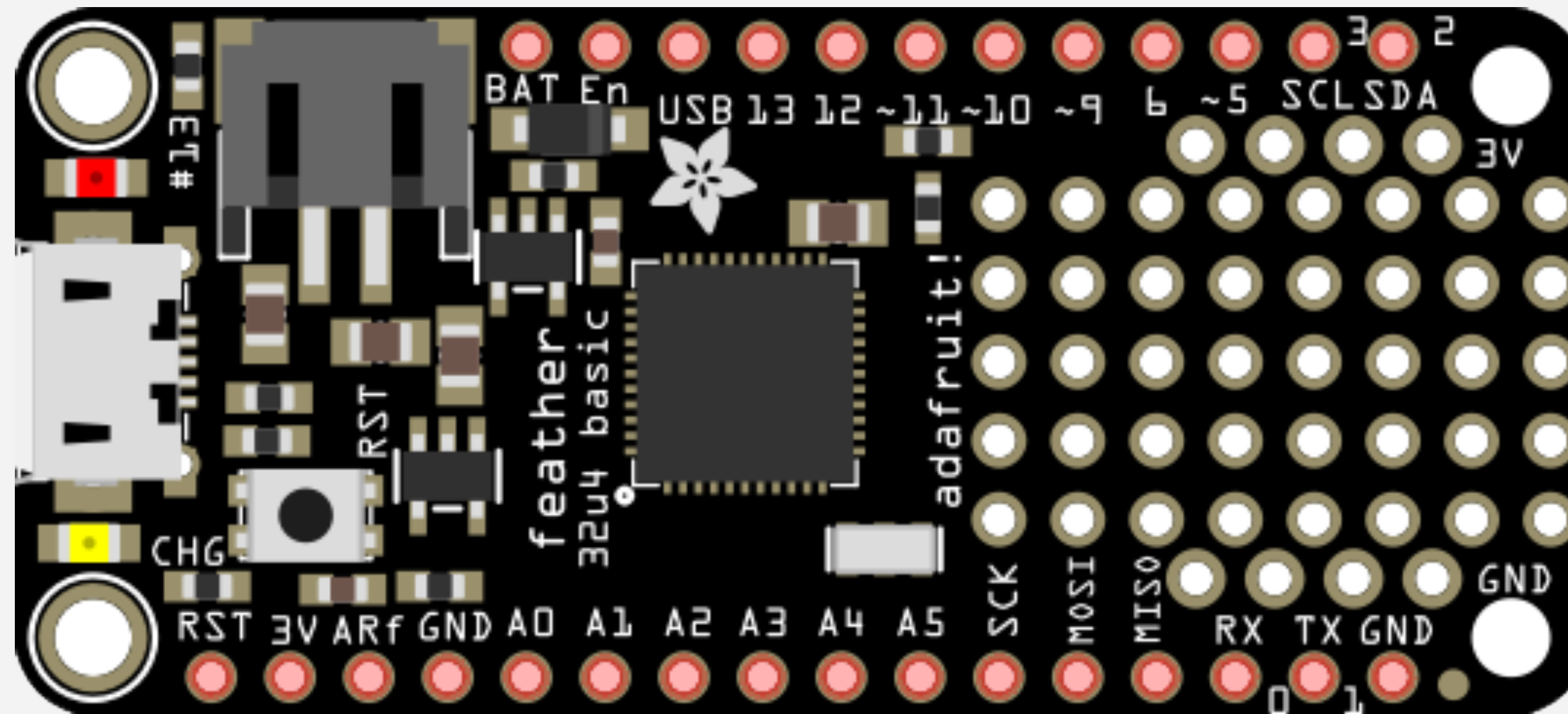

**Analog Input Pins**

# Analog Input


The inputs on the Arduino read voltage.


All inputs need to be thought of in terms of voltage differentials.


Unlike digital inputs, analog inputs convert differences in voltage levels into a number from 0-1024

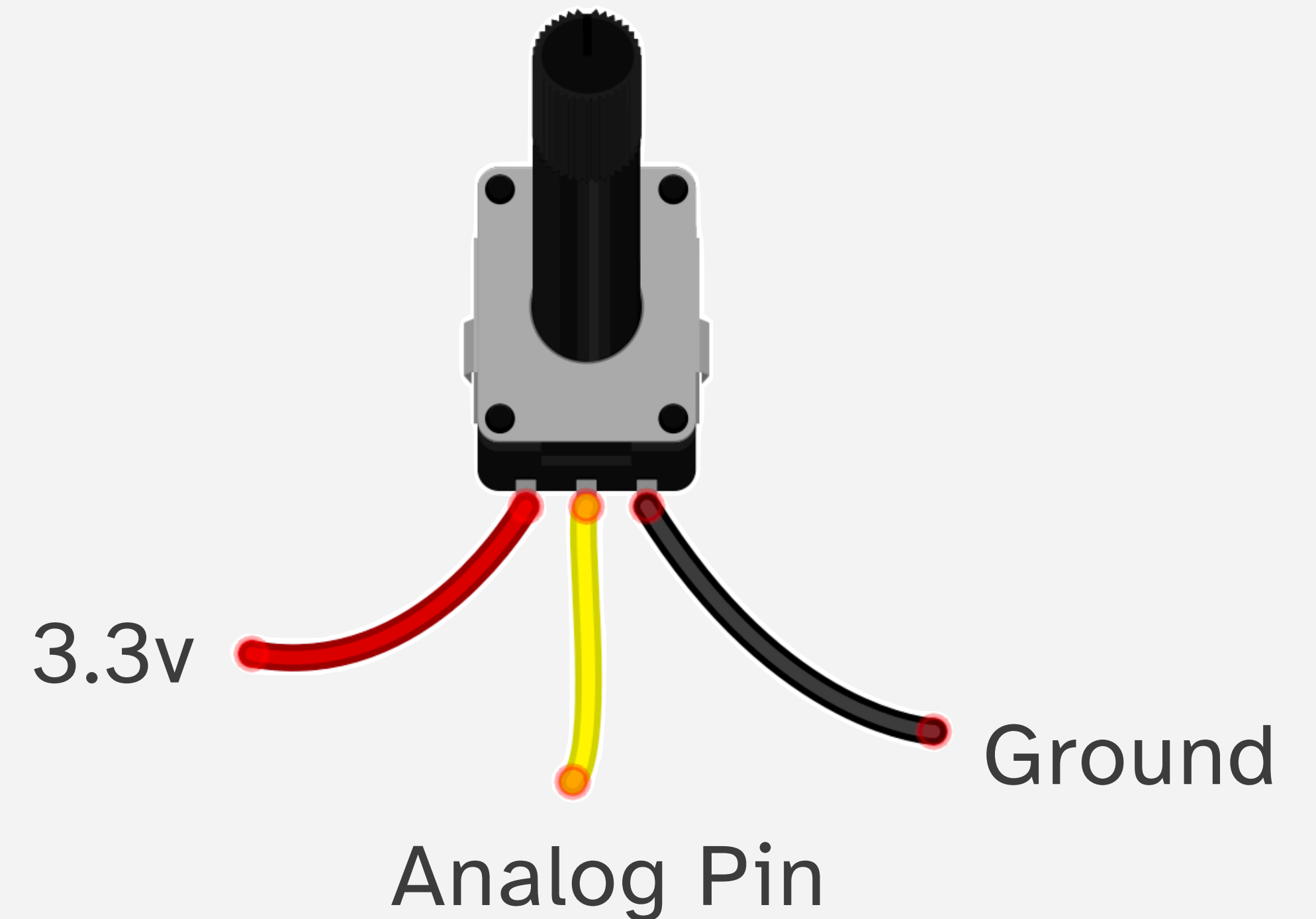
# Analog Input


The potentiometer is the easiest analog input to use. It has three connections.



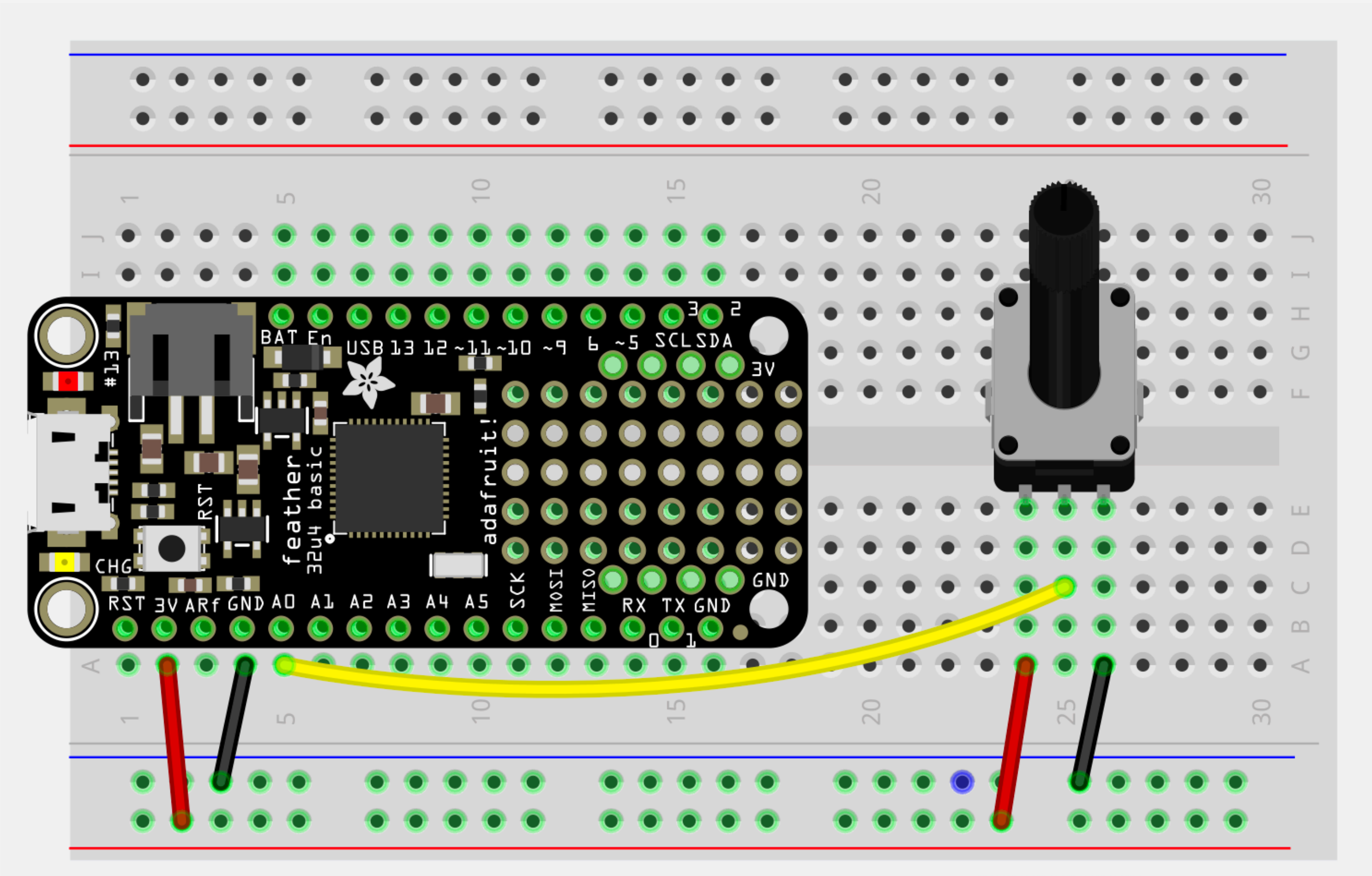

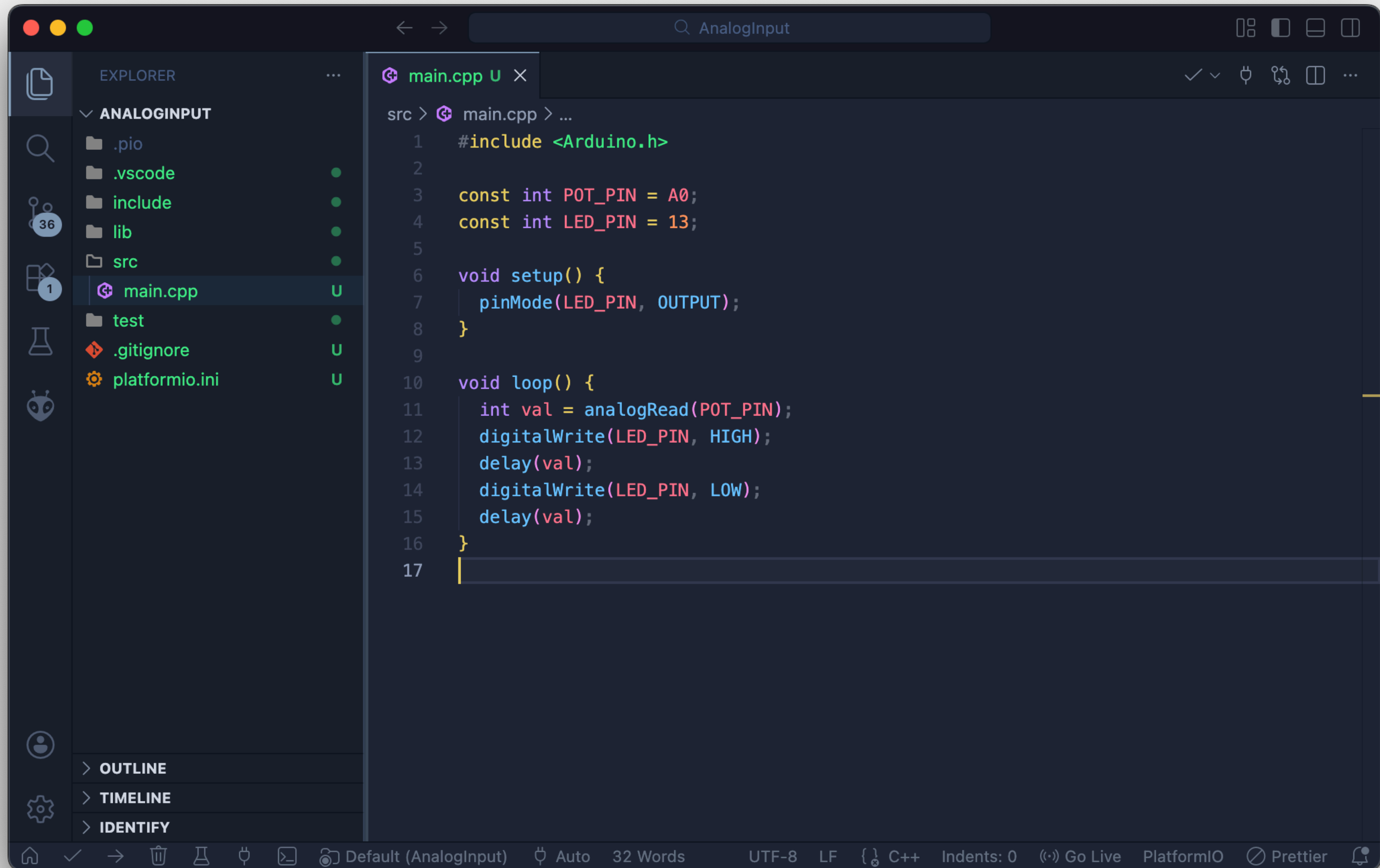

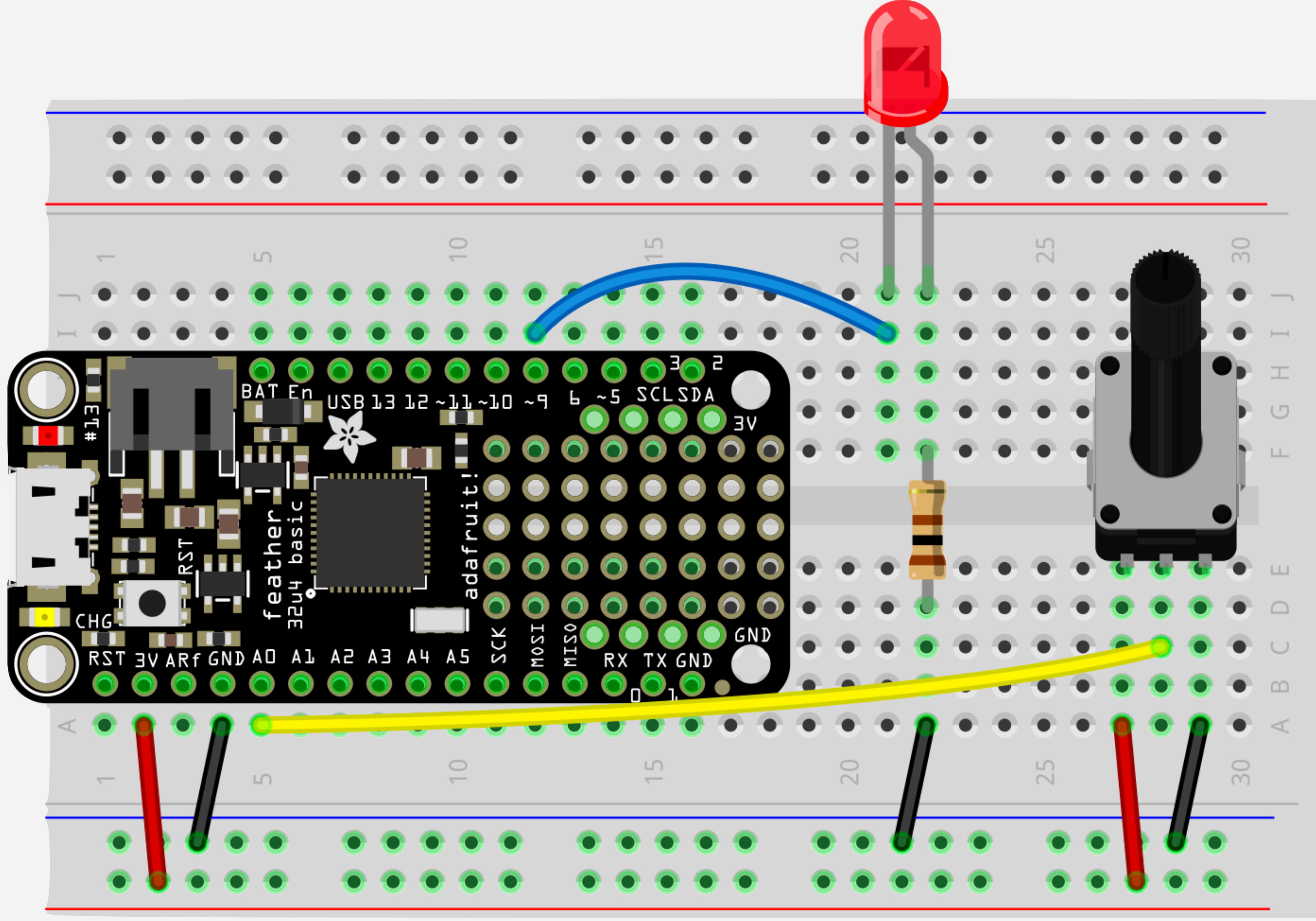

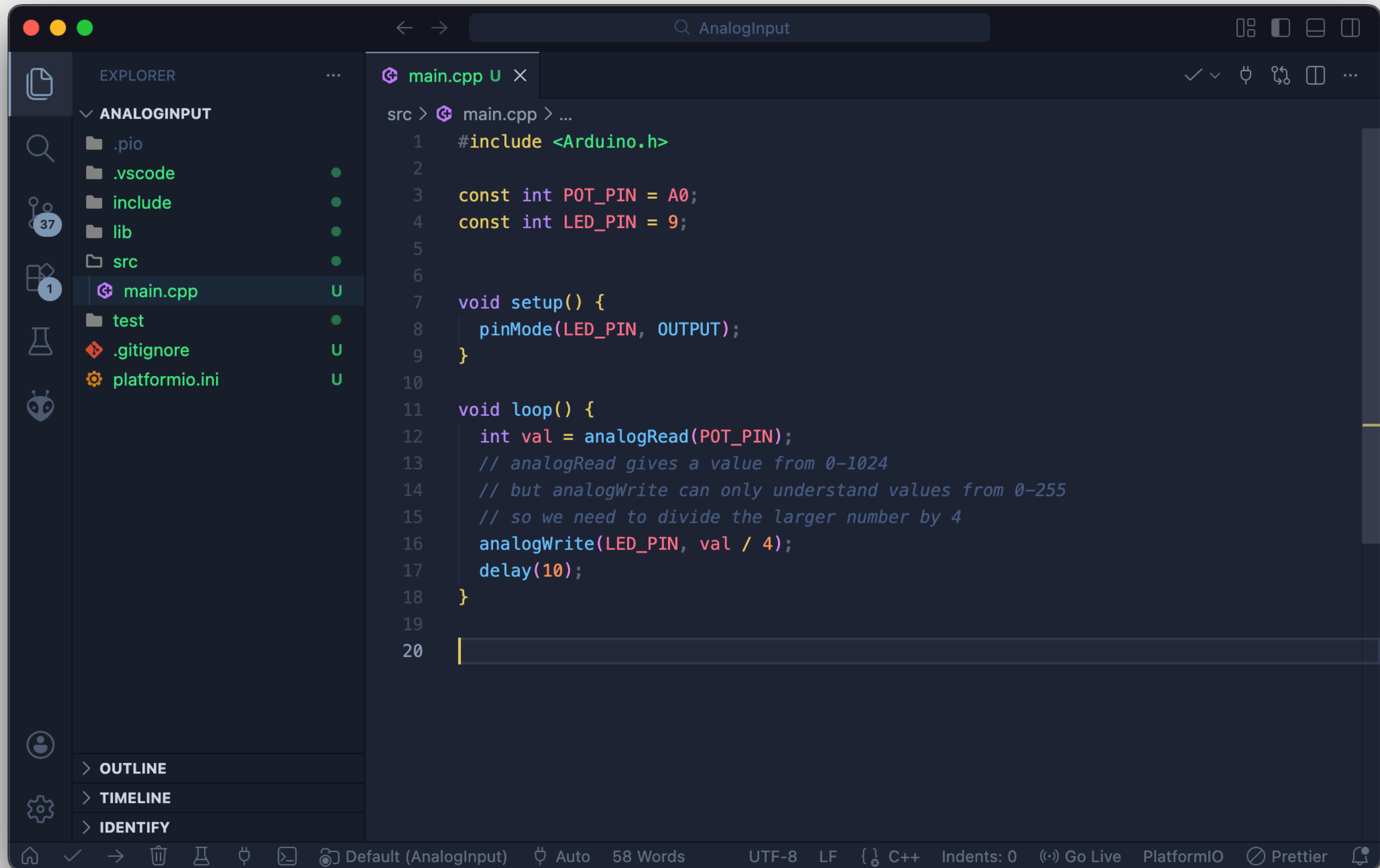



# Try...

...having the LED make a pattern when the button is pressed.

...controlling two LEDs with one button.

...using two buttons that both must be pressed for the LED to turn on.

...using buttons from the bin in the FabLab.